



وزارة التعليم العالي والبحث العلمي
الجامعة التقنية الشمالية
المعهد التقني الموصل



الحقيبة التعليمية

القسم العلمي: التقنيات الالكترونية والاتصالات

اسم المقرر: دوائر التيار المستمر

المرحلة / المستوى: الأولى / الاول

الفصل الدراسي: الأول

السنة الدراسية: 2024-2025



اسم المقرر:	دوائر التيار المستمر
القسم:	التقنيات الالكترونية
الكلية:	المعهد التقني الموصل
المرحلة / المستوى	الأولى \ الاول
الفصل الدراسي:	الاول
عدد الساعات الاسبوعية:	نظري 2 عملي 2
عدد الوحدات الدراسية:	4
الرمز:	ETM100
نوع المادة	نظري - عملي - كلهما √
هل يتوفر نظير للمقرر في الاقسام الاخرى	----
اسم المقرر النظير	
القسم	
رمز المقرر النظير	
معلومات تدريسي المادة	
اسم مدرس (مدرسي) المقرر:	سماء خالد غانم
اللقب العلمي:	مدرس مساعد
سنة الحصول على اللقب	2023
الشهادة :	ماجستير
سنة الحصول على الشهادة	2015
عدد سنوات الخبرة (تدريس)	5 سنوات

الوصف العام للمقرر

في هذا المقرر يتم التعرف على وحدات النظام الدولية ومضاعفاتها و مكونات الدائرة الكهربائية و تطبيق القوانين الخاصة بالدوائر الكهربائية مثل قانون اوم و قانون كيرشوف. وكذلك التميز بين أنواع الربط المختلف للمقاومات وكيفية إيجاد المقاومة المكافئة لتلك الدوائر الكهربائية. بالإضافة الى تحليل الدوائر الكهربائية المعقدة باستخدام بعض النظريات مثل نظرية ثفنن ونظرية نورتن.

الاهداف العامة

- ان يكون قادرا على فهم وتطبيق القوانين الخاصة في الدائرة الكهربائية
- ان يكون قادرا على تطبيق النظريات الخاصة في الدائرة الكهربائية

الأهداف الخاصة

- ان يكون قادرا على تطبيق قانون اوم وإيجاد الفولتية والتيار والقدرة في دائرة الكهربائية .
- ان يتعلم كيفية حساب المقاومة المكافئة في الربط التوالي والتوازي والمختلط .
- ان يكون قادرا على تحويل الربط من النجمي الى المثلثي و بالعكس وإيجاد المقاومة المكافئة.
- ان يتعرف على قانون كيرشوف وكيفية تحليل الدائرة باستخدام قانون كيرشوف
- ان يتعلم كيفية الحل بطريقة mesh الذي يعتمد على قانون كيرشوف للفولتيات.
- ان يكون قادرا على تحليل الدوائر الكهربائية المعقدة باستخدام بعض النظريات مثل نظرية ثفنن و نورتن و النظرية التراكمية.
- ان يكون قادرا على كيفية تحويل مصدر الفولتية و التيار من احدهما الى الاخر لتسهيل حل الدائرة وإيجاد التيار او الفولتية في أي مقاومة في الدائرة الكهربائية .
- ان يتعرف على نظرية نقل اعظم قدرة ممكنة وكيفية اشتقاقها وإيجادها في الدائرة الكهربائية

الأهداف السلوكية او نواتج التعلم

- ان يكون للطالب القدرة على التفكير وحل المشكلات والدوائر الكهربائية.
- ان يكون للطالب القدرة على التحليل والتفكير العلمي عن طريق تطبيق القوانين.
- ان يكون القدرة على الاستقصاء العلمي في ما يتعلق بجوانب الدوائر الكهربائية
- ان يكون التمسك بأخلاقيات المهنة والقدرة على ابداء الكفاءة المهنية

المتطلبات السابقة

- ان يكون للطالب معرفة بسيطة عن مكونات الدائرة الكهربائية وتطبيق قانون اوم من خلال إيجاد الفولتية والتيار
- ان يكون الطالب قادرا على حل المعادلات الحسابية الرياضية.

الأهداف السلوكية او مخرجات التعليم الأساسية		
ت	تفصيل الهدف السلوكي او مخرج التعليم	آلية التقييم
1	1 ان يكون للطالب القدرة على التفكير وحل المشكلات والدوائر الكهربائية.	المناقشة اثناء المحاضرة والامتحانات اليومية والشهرية
2	ان يكون للطالب القدرة على التحليل والتفكير العلمي عن طريق تطبيق القوانين. -	الواجبات الصفية والمنزلية
3	ان يكون القدرة على الاستقصاء العلمي في ما يتعلق بجوانب الدوائر الكهربائية -	امتحان نهاية الكورس.

أساليب التدريس (حدد مجموعة متنوعة من أساليب التدريس لتناسب احتياجات الطلاب ومحتوى المقرر)

مبررات الاختيار	الاسلوب او الطريقة
ليكون هناك تواصل بين الطالب والتدريسي بصورة مباشرة مع استخدام السبورة التقليدية لوجود مسائل رياضية في مادة الدوائر الكهربائية التي تحتاج الى الحل خطوة بخطوة حيث تعتبر احد الطرق الحديثة المستخدمة لمواكبة التكنولوجيا عن طريق استخدام برنامج classroom و دعمها بالفديوهات و الملفات الخاصة بالمحاضرات.	1.لقاء المحاضرة
فسح المجال للسؤال و تبادل الآراء بين التدريسي و الطلاب لتطوير مهارات الطالب في القراءة في مجاله والبحث	2.التعليم المدمج
	3.المناقشة
	4.التقارير

الفصل الأول

الفصل الأول						
Basics of electric circuits				الوقت		عنوان الفصل
طرق القياس	التقنيات	طريقة التدريس	العنوان الفرعي	العملي	النظري	التوزيع الزمني
	عرض تقديمي، شرح، أسئلة وأجوبة، مناقشة	محاضرة	مقدمة عن المقرر، أهداف التعلم، محتوى المقرر	2	2	الأسبوع الأول
	عرض تقديمي، شرح، أسئلة وأجوبة، مناقشة	محاضرة	العناوين الفرعية	2	2 ساعة	الأسبوع الثاني
			Electrical Quantities and Units			
			Multiple and Submultiple of the Internarial System Units (SI):			
			Electrical Circuit Components Ohm's law			
			Electrical Power			
			Resistor Power Absorption			
	عرض تقديمي، شرح، أسئلة وأجوبة، مناقشة	محاضرة	Resistance and Resistivity	2	2	الأسبوع الثالث
			Resistor temperature coefficient			

الفصل الثاني

Equivalent Resistance				الوقت		عنوان الفصل
طرق القياس	التقنيات	طريقة التدريس	العنوان الفرعي	العملي	النظري	التوزيع الزمني
	عرض تقديمي، شرح، أسئلة وأجوبة، مناقشة	محاضرة	Series Circuit	2	2	الأسبوع الرابع
			Voltage divider's law			
			Parallel circuit			
			Current divider's law			
	عرض تقديمي، شرح، أسئلة وأجوبة، مناقشة	محاضرة	Series-Parallel combination	2	2	الأسبوع الخامس
			examples			
	عرض تقديمي، شرح، أسئلة وأجوبة، مناقشة	محاضرة	Wye-delta transformations	2	2	الأسبوع السادس
			example			
	عرض تقديمي، شرح، أسئلة وأجوبة، مناقشة	محاضرة	حل امثلة متنوعة عن جميع أنواع ربط الدوائر الكهربائية	2	2	الأسبوع السابع

الفصل الثالث

DC Circuit Analysis						
عنوان الفصل		الوقت		التوزيع الزمني		
النظري		العملي		العنوان الفرعي		
طرق القياس		التقنيات		طريقة التدريس		
	2 ساعة	2	الأسبوع الثامن	العناوين الفرعية		
				`Kirchhoff's law method (Branch current method)		
				Examples		
	2	2	الأسبوع التاسع	Mesh method (Maxwell current loop method)		
				Examples		

الفصل الرابع

Circuit Theorems					الوقت		عنوان الفصل
	عرض تقديمي، شرح، أسئلة وأجوبة، مناقشة	محاضرة	العناوين الفرعية		2	2 ساعة	
			Superposition theorem	Superposition theorem			الأسبوع العاشر
			Examples				
	عرض تقديمي، شرح، أسئلة وأجوبة، مناقشة	محاضرة	Thevenin's theorem	Thevenin's theorem	2	2	الأسبوع الحادي عشر
			Examples				
	عرض تقديمي، شرح، أسئلة وأجوبة، مناقشة	محاضرة	Norton's Theorem	Norton's Theorem	2	2	الأسبوع الثاني عشر
			Examples				
	عرض تقديمي، شرح، أسئلة وأجوبة، مناقشة	محاضرة	Source transformations	Source transformations	2	2	الأسبوع الثالث عشر
			Examples				
	عرض تقديمي، شرح، أسئلة وأجوبة، مناقشة	محاضرة	maximum power transfer	maximum power transfer	2	2	الأسبوع الرابع عشر
			Examples				
	عرض تقديمي، شرح، أسئلة وأجوبة، مناقشة	محاضرة	حل امثلة متنوعة على النظريات		2	2	الأسبوع الخامس عشر

المحتوى العلمي

خارطة القياس المعتمدة

عدد الفقرات	الأهداف السلوكية						الأهمية النسبية	عناوين الفصول	المحتوى التعليمي
	التقييم	التحليل	التطبيق	الفهم	المعرفة	النسبة			
5	1	1	1	1	1		%10		الفصل الاول
10	2	2	2	2	2		%35		الفصل الثاني
5	1	1	1	1	1		%20		الفصل الثالث
10	2	2	2	2	2		%35		الفصل الرابع
									الفصل الخامس
									الفصل السادس
30	6	6	6	6	6		%100		المجموع

المحتويات (لكل فصل في المقرر)

رقم المحاضرة: الثانية	عنوان المحاضرة:
اسم المدرس:	units System and ohm's law
الفئة المستهدفة :	سماء خالد غانم
الهدف العام من المحاضرة :	المرحلة أولى\الفصل الدراسي الأول\ قسم التقنيات الإلكترونية\المعهد التقني الموصل
الأهداف السلوكية او مخرجات التعلم:	1- ان يتعرف الطالب على وحدات ومكونات الدائرة الكهربائية 2- ان يفهم الطالب قانون اوم
استراتيجيات التيسير المستخدمة	1- ان يتعرف الطالب على وحدات القياس الخاصة في الدائرة الكهربائية 2- ان يكون الطالب قادرا على تطبيق قانون اوم
المهارات المكتسبة	1. القاء المحاضرة 2. التعليم المدمج 3. المناقشة 4. التقارير
طرق القياس المعتمدة	1- سيتمكن الطالب من معرفة وحدات النظام الدولي والمكونات الخاصة في الدائرة الكهربائية 2- سيكون الطالب قادرا على إيجاد الفولتية و التيار و القدرة في الدائرة الكهربائية البسيطة
	امتحانات يومية-امتحانات شهرية

الاسئلة القبليه

- 1- What is the units of voltage, current, Resistance?
- 2- What is the equation of ohm's law?

المحتوى العلمي

- Electrical Quantities and Units
- Multiple and Submultiple of the Internarial System Units (SI):
- Electrical Circuit Components
- Ohm's law
- Electrical Power
- Resistor Power Absorption

Electrical Quantities and Units:

Table 1: Electrical quantities and units

Electrical Quantity	Symbol	Measuring Unit	Symbol
Voltage	V or E	Volt	v
Current	I or i	Ampere	A
Resistance	R	Ohm	Ω
Conductance	G	Siemen	S or $\mathcal{U}$
Capacitance	C	Farad	F
Inductance	L	Henry	H
Power	P	Watts	w
Impedance	Z	Ohm	Ω
Frequency	f	Hertz	Hz

Multiple and Submultiple of the Internarial System Units (SI):

Here is a huge range of values encountered in electrical and electronic engineering between a maximum value and a minimum value of a standard electrical unit. For example, resistance can be lower than 0.001Ω or higher than $1,000,000\Omega$. By using multiples and submultiples of the standard unit we can avoid having to write too many zeros to define the position of the decimal point. The table (2) shows the Multiple and Submultiple Internarial System Units (SI).


Table (2) Internarial System Units (SI)

Prefix	Symbol	Multiplier and Submultiple	Power of Ten
kilo	k	1,000	10^3
Mega	M	1,000,000	10^6
Giga	G	1,000,000,000	10^9
Terra	T	1,000,000,000,000	10^{12}
centi	c	0.01	10^{-2}
milli	m	0.001	10^{-3}
micro	μ	0.000001	10^{-6}
nano	n	0.000000001	10^{-9}
pico	p	0.000000000001	10^{-12}

Example: Show multiples or submultiple of International System units for each one of the following:

- $V = 1\text{ kV} = 1 \times 10^3 = 1 \times 1000 = 1,000 \text{ V}$.
- $I = 3\text{ mA} = 3 \times 10^{-3} = 3 \times 0.001 = 0.003 \text{ A}$.
- $A = 5\text{ mm}^2 = 5 \times (10^{-3})^2 = 5 \times 10^{-6} = 0.000005\text{ m}^2$

Electrical Circuit Components

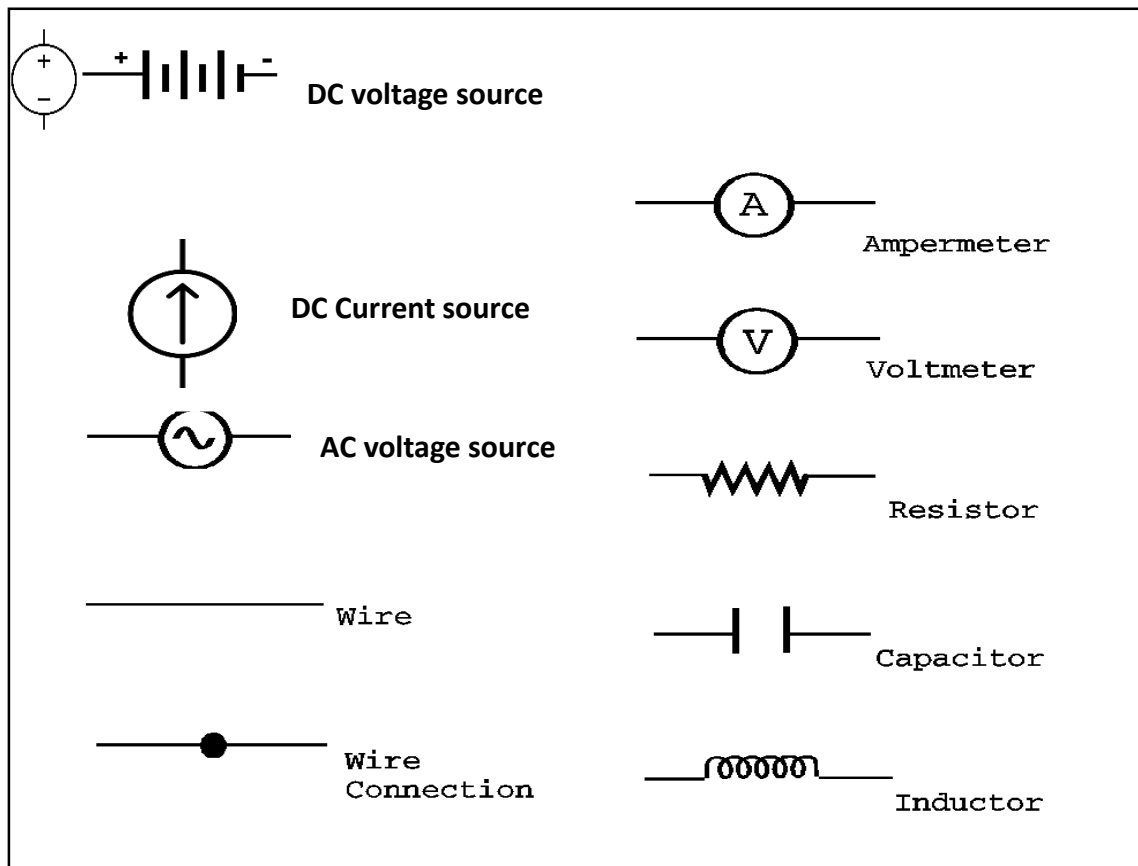

Ohm's law

Ohm's law states that the voltage v across a resistor is directly proportional to the current i flowing through the resistor.


$$V \propto I$$

$$V = R I$$

V : voltage (volt)

I : current (Ampere)

R : Resistance (ohm)

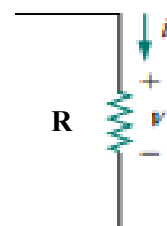

Ohm's Law Triangle


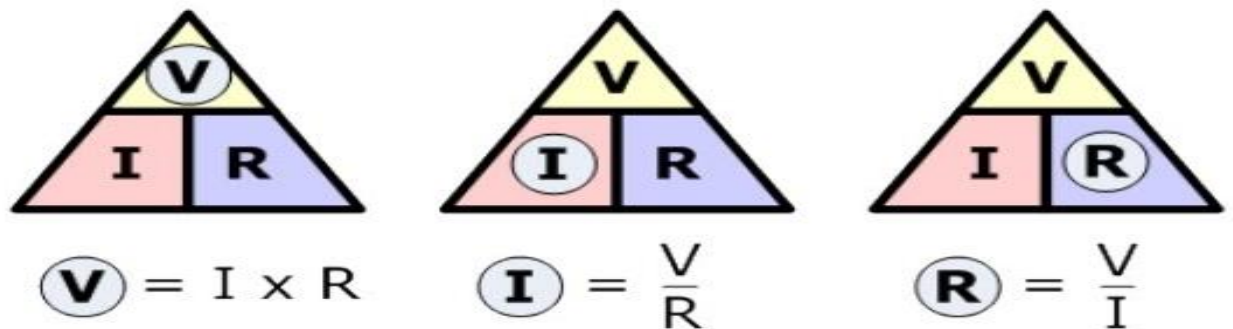


Figure below shows the relation between the voltage and current of resistance which there are two types of resistances:

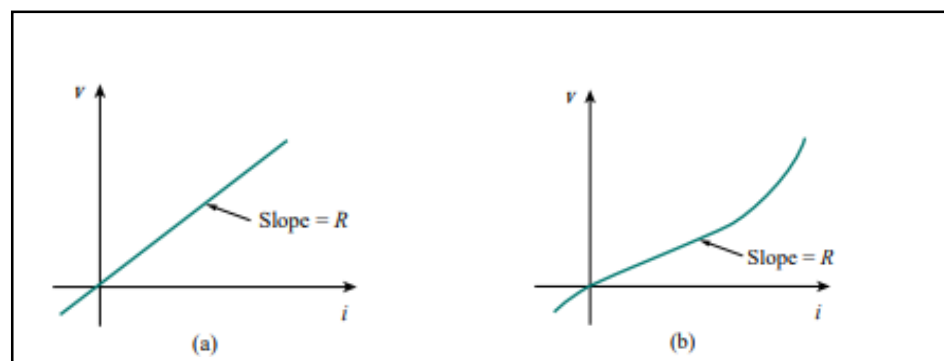- 1- linear resistance (ohm's law)
- 2- non-linear resistance.



The i-v characteristic of: (a) a linear resistor, (b) a nonlinear resistor.

-Most of conductors are linear resistance so can be used the ohm's law while in non-linear resistance cannot used ohm's law such as semi-conductor.

-The inverse of the resistance is often useful. It is called conductance and quantity symbol is G. The unit of conductance is Siemen (S) or (Ω).

$$G = \frac{1}{R}$$

Electrical Power:

Power (P) in the electrical circuit is given by product the voltage (V) and the current (I). The unit of the power is watt (w).

$$P=V * I$$

Example The current flowing through a resistance is 0.8 A. when the voltage source 20v is applied. Find

- 1) The resistance
- 2) the conductance
- 3) The total power

Solution:

- 1) $R = \frac{v}{I} = \frac{20}{0.8} = 25\Omega$
- 2) $G = \frac{1}{R} = \frac{1}{25} = 0.04 S$
- 3) $P = V * I = 20 * 0.8 = 16w$

Example In the circuit shown in figure below, calculate the current, the conductance, and the power.


Solution:

$$\text{the current is } i = \frac{V}{R} = \frac{30}{5 \times 10^3} = 0.006A = 6 \text{ mA}$$

$$\text{The conductance is } G = \frac{1}{R} = \frac{1}{5 \times 10^3} = 0.00002S = 0.2 \text{ mS}$$

$$P = V * I = 30 * (6 \times 10^{-3}) = 180 \text{ mW.}$$

Figure (1.2)

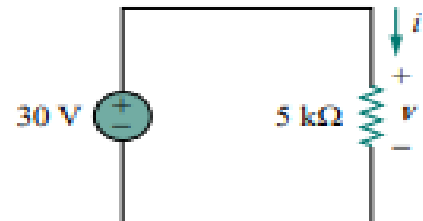

Resistor Power Absorption:

There are two equations:

$$V = I * R \dots \dots \dots (1)$$

$$P = V * I \dots \dots \dots (2)$$

When substituting Eq. (1) in Eq. (2)

$$P = I * R * I = I^2 * R$$

Or

$$P = v * \frac{v}{R} = \frac{v^2}{R}$$

The resistor power absorption is


$$P = I^2 * R \quad \text{Or} \quad P = \frac{v^2}{R}$$

الأسئلة البعيدة

1- Show multiples or submultiple of Internarial System units for each one of the following:

- C= 100 μ F
- P= 1pw
- F= 1MHz
- V= 7cm³

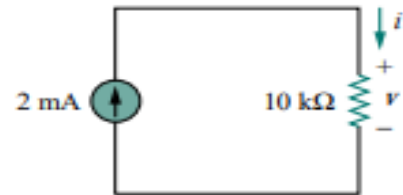2- For the circuit shown below, calculate the voltage v, the conductance G, and the power p. (Answer: 20 V, 100 μ S, 40 mW)



رقم المحاضرة: الثالثة	عنوان المحاضرة:
Resistivity and Resistor temperature coefficient	اسم المدرس:
سماء خالد غانم	المرحلة أولى\الفصل الدراسي الأول\ قسم التقنيات الإلكترونية\المعهد التقني الموصل
الهدف العام من المحاضرة :	1-ان يتعرف الطالب على العوامل المؤثرة على المقاومة 2-ان يفهم الطالب تأثير الحرارة على المقاومة .
الأهداف السلوكية او مخرجات التعلم:	1-ان يفهم الطالب العوامل المؤثرة على المقاومة 2- ان يكون قادرا الطالب على تطبيق القوانين الخاصة بالمعامل الحراري للمقاومة
استراتيجيات التيسير المستخدمة	1. القاء المحاضرة 2. التعليم المدمج 3. المناقشة 4. التقارير
المهارات المكتسبة	3- سيتمكن الطالب من تطبيق القانون الخاص لإيجاد المقاومة اعتمادا على الطول و المساحة و المقاومة النوعية للمادة 4- سيكون الطالب قادرا على إيجاد قيمة المقاومة قبل او بعد تعرضها لتغير الحرارة بالاعتماد على المعامل الحراري للمادة
طرق القياس المعتمدة	امتحانات يومية-امتحانات شهرية

الاسئلة القبليه

- 1- What is the factors affecting resistance?
- 2- What is the effect of temperature on resistance ?

المحتوى العلمي

- Resistance and Resistivity
- Resistor temperature coefficient

محتويات المحاضرة

Resistance and Resistivity

The resistance of the conductor of uniform cross section is depend on:

- 1) The type of material (Resistivity).
- 2) Length
- 3) Cross section area
- 4) The temperature.

Hence:

$$R = \rho \frac{l}{A} \quad \text{At } (20^\circ\text{C})$$

R: Resistance (Ω)

ρ : Resistivity ($\Omega \cdot \text{m}$)

l : length (m)

A: cross section Area (m^2)

Resistivity is a fundamental property of material, when the value of the resistivity is very small that means the material is good conductor (conductor material), but when the value of resistivity is very big that means the material is low conductor (isolator material). Table 3 represents the resistivity of different materials.

Table 3 represents the resistivity of materials.

Resistivities at 20°C	
Material	Resistivity ($\Omega \cdot \text{m}$)
Aluminum	2.82×10^{-8}
Copper	1.72×10^{-8}
Gold	2.44×10^{-8}
Nichrome	$150. \times 10^{-8}$
Silver	1.59×10^{-8}
Tungsten	5.60×10^{-8}

Example Find the resistance of 20 C° of annealed copper bar 3mm in length and 1.5cm² in rectangular cross section area. (Resistivity = $1.72 \times 10^{-8} \Omega \cdot \text{m}$)

Solution:

$$R = \rho \frac{l}{A}$$

$$R = 1.72 \times 10^{-8} \frac{3 \times 10^{-3}}{1.5 \times (10^{-2})^2}$$

$$R = 3.44 \times 10^{-7} \Omega$$

Resistor temperature coefficient:

The resistance of best conducting material increases almost linearly with temperature over range of normal operating temperature.

$$R_2 = R_1(1 + \alpha_0(T_2 - T_1))$$

$$R_0 = R_T(1 - \alpha_T T)$$

$$R_T = R_0(1 + \alpha_0 T)$$

$$\alpha_T = \frac{\alpha_0}{1 + \alpha_0 * T}$$

R_1 : resistance at lower temperature T_1

R_2 : resistance at higher temperature T_2

R_T : resistance at temperature T

R_0 : resistance at zero temperature $0C^0$

α_0 : resistor temperature coefficient at $0C^0$

α_T : resistor temperature coefficient at TC^0 (Ω/C^0)

Example coil resistance is 3.146Ω at $40C^0$ and 3.717 at $100C^0$. Find

- 1) Resistor temperature coefficient at $0C^0$.
- 2) Coil resistance at $0C^0$.
- 3) Resistance temperature coefficient at $40C^0$.

Solution:

$$(1) R_2 = R_1(1 + \alpha_0(T_2 - T_1))$$

$$3.717 = 3.146(1 + \alpha_0(100 - 40))$$

$$3.717 = 3.146(1 + \alpha_0 * 60)$$

$$3.717 = ((3.146 * 1) + (3.146 \alpha_0 * 60))$$

$$3.717 = 3.146 + 188.76 \alpha_0$$

$$3.717 - 3.146 = 188.76 \alpha_0$$

$$0.571 = 188.76 \alpha_0$$

$$\alpha_0 = \frac{0.571}{188.76} = 0.003 \Omega/C^0$$

$$(2) R_T = R_0(1 + \alpha_0 T)$$

$$3.146 = R_0(1 + 0.003 * 40)$$

$$3.146 = 1.12 R_0$$

$$R_0 = \frac{3.146}{1.12} = 2.825 \Omega$$

$$(3) \alpha_T = \frac{\alpha_0}{1 + \alpha_0 * T}$$

$$\alpha_{40} = \frac{0.003}{1 + 0.003 * 40} = 0.0026 \Omega/C^0$$

الأسئلة البعيدة

- 1- Find the cross-section area of the aluminum wire at $20C^0$ that has length of 1Km and the resistance is 0.002Ω . (Resistivity $= 2.82 * 10^{-8} \Omega.m$). (answer: **$A=0.0141m^2$**)
- 2- Copper coil resistance is 100Ω at $20C^0$. Calculate it is resistance at $100C^0$. If the resistance temperature coefficient at $20 C^0$ is $0.004 \Omega/C^0$. (answer: **$R_2=134.4\Omega$**)

المحتويات (لكل فصل في المقرر)

رقم المحاضرة:الرابعة	عنوان المحاضرة:
اسم المدرس:	سماء خالد غانم
الفئة المستهدفة :	المرحلة أولى\الفصل الدراسي الأول\ قسم التقنيات الإلكترونية\المعهد التقني الموصل
الهدف العام من المحاضرة :	ان يتعرف الطالب على ربط التوالي والتوازي في دوائر الكهربائية
الأهداف السلوكية او مخرجات التعلم:	1-ان يكون الطالب قادرا على معرفة التميز بين ربط التوالي وربط التوازي في الدوائر الكهربائية 2-ان يكون الطالب قادرا على تطبيق القوانين الخاصة لكل من مقسم الفولطية في ربط التوالي ومقسم التيار في ربط التوازي
استراتيجيات التيسير المستخدمة	1.لقاء المحاضرة 2.التعليم المدمج 3.المناقشة 4.التقارير
المهارات المكتسبة	1-سيتمكن الطالب من تطبيق القوانين الخاص لكل من ربط الدائرة التوالي وربط دائرة التوازي

2- سيكون الطالب قادرا على إيجاد الفولطية لكل مقاومة في ربط التوالي باستخدام مقسم الفولطية وإيجاد التيار لكل مقاومة في ربط التوازي باستخدام مقسم التيار	
امتحانات يومية-امتحانات شهرية	طرق القياس المعتمدة

الاسئلة القبليه

- 1) If number of resistances connection in series write total voltage, current laws .
- 2) If number of resistances connection in Parallel wrights total voltage , current laws

المحتوى العلمي

- Series Circuit
- Voltage divider's law
- Parallel circuit
- Current divider's law

محتويات المحاضرة

Series Circuit

As shown in figure below, the two resistors are in series which has characteristic as following:

- 1) The R_1 and R_2 have the same current and equal i

2)

$$V_1 = i * R_1$$

$$V_2 = i * R_2$$

- 3) By using KVL to loop (Clockwise direction) we have

$$-V + V_1 + V_2 = 0$$

$$V = V_1 + V_2$$

- 4) The equivalent resistance:



$$R_{eq} = R_1 + R_2$$

For N resistor in Series

$$R_{eq} = R_1 + R_2 + R_3 + R_4 + \dots + R_N$$

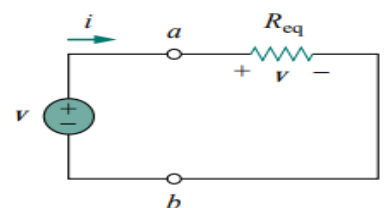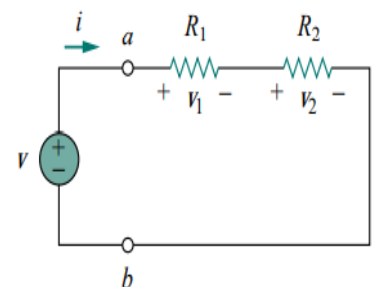5)

$$V = R_{eq} * i \text{ as shown in figure}$$



Voltage divider's law:

$$V_1 = i * R_1 \text{ -----(1)}$$

$$V = R_{eq} * i \text{ -----(2)}$$

$$R_{eq} = R_1 + R_2 \text{ -----(3)}$$

Substituting Eq. (2) and Eq. (3) in Eq. (1)

$$V_1 = \frac{V}{R_1 + R_2} * R_1$$


$$V_2 = \frac{V}{R_1 + R_2} * R_2$$

$$V_N = \frac{V}{R_{eq}} * R_N$$

N: represent the resistance

Example2: From the circuit shown in figure below, find

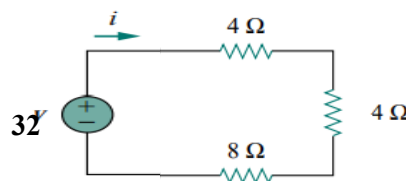- 1) The equivalent resistance.
- 2) the current through each resistance
- 3) the voltage of 8Ω using voltage divider's law.



Solution:

$$1) R_{eq} = R_1 + R_2 + R_3$$

$$R_{eq} = 4 + 4 + 8 = 16 \Omega$$

$$2) V = R_{eq} * i$$

$$32 = 16 * i$$

$$i = \frac{32}{16}$$

$$i = 2A \quad \text{which } i = I_{4\Omega} = I_{4\Omega} = I_{8\Omega} \text{ (Series Connection)}$$

$$3) V_N = \frac{V}{R_{eq}} * R_N$$

$$V_{8\Omega} = \frac{32}{4 + 4 + 8} * 8 = 16V$$

Example: For the circuit shown in figure below, find the voltage source v .

Solution:

$$V = R_{eq} * i$$

$$R_{eq} = R_1 + R_2 + R_3$$

$$R_{eq} = 3 + 4 + 5 = 12 \, \Omega$$


$$V_{3\Omega} = i * R_{3\Omega}$$

$$6 = i * 3$$

$$i = 2A$$


$$V = R_{eq} * i$$

$$V = 12 * 2 = 24V$$

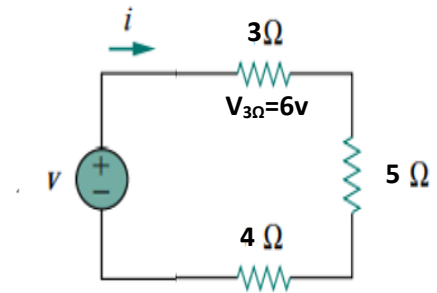

Parallel circuit

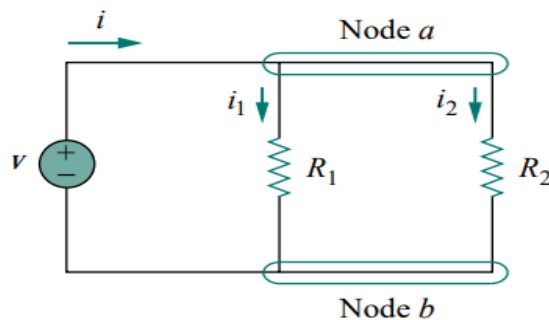As shown in figure below, the two resistors are in parallel which has characteristic as following:



- 1) The R_1 and R_2 have the same voltage and equal V (V = Voltage source).

$$V = V_{R1} = V_{R2}$$

$$2) \quad i_1 = \frac{V}{R_1}$$

$$i_2 = \frac{V}{R_2}$$

- 3) By using KCL at node a (Clockwise direction) we have

$$i = i_1 + i_2$$

- 4) The equivalent resistance of two resistance:

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$\frac{1}{R_{eq}} = \frac{R_2 + R_1}{R_1 R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

For N resistor in parallel

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \dots \dots \dots \frac{1}{R_N}$$

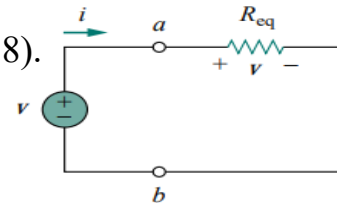5) $V = R_{eq} * i$ as shown in figure (2.8).



Current divider's law:

$$i_1 = \frac{V}{R_1} \text{-----(1)}$$

$$V = R_{eq} * i \text{-----(2)}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} \text{-----(3)}$$


Substituting Eq. (2) and Eq. (3) in Eq. (1)

$$i_1 = \frac{i}{R_1 + R_2} * R_2$$

$$i_2 = \frac{i}{R_1 + R_2} * R_1$$

Example: for the circuit in figure , find

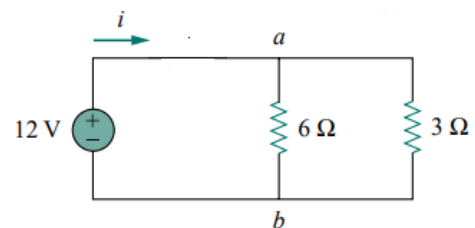- 1) The equivalent resistance
- 2) Total current
- 3) The current of each resistance



Solution:

$$1) R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_{eq} = \frac{3 * 6}{3 + 6}$$

$$R_{eq} = \frac{18}{9} = 2\Omega$$

$$2) V = R_{eq} * i$$

$$12 = 2 * i$$

$$i = 6A$$


$$3) i_1 = \frac{V}{R_1}$$

$$i_1 = \frac{12}{6} = 2A$$

$$i_2 = \frac{V}{R_2}$$

$$i_2 = \frac{12}{3} = 4A$$

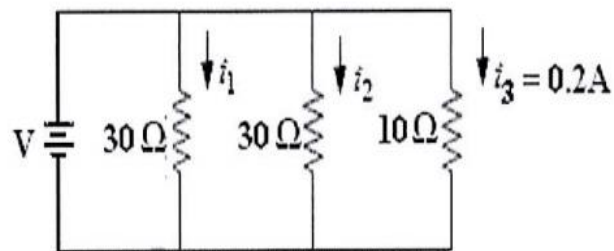Example : Find V (voltage source) of the circuit shown in figure below, if the $i_3 = 0.2A$, then find total current I and the equivalent resistance.



Solution:

$$i_3 = \frac{V}{R_3}$$

$$0.2 = \frac{V}{10}$$

$$V = 0.2 * 10 = 2V$$

$$i_1 = \frac{V}{R_1}$$

$$i_1 = \frac{2}{30} = 0.06 A$$

$$i_2 = \frac{V}{R_2}$$

$$i_2 = \frac{2}{30} = 0.06A$$

$$i = i_1 + i_2 + i_3$$

• total current

$$i = 0.2 + 0.06 + 0.06 = 0.32A$$

• equivalent resistance

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{eq}} = \frac{1}{30} + \frac{1}{30} + \frac{1}{10}$$


$$\frac{1}{R_{eq}} = \frac{1}{30} + \frac{1}{30} + \frac{3}{30}$$

$$\frac{1}{R_{eq}} = \frac{5}{30} = \frac{1}{6}$$


$$R_{eq} = 6\Omega$$

الاختبار البعدي

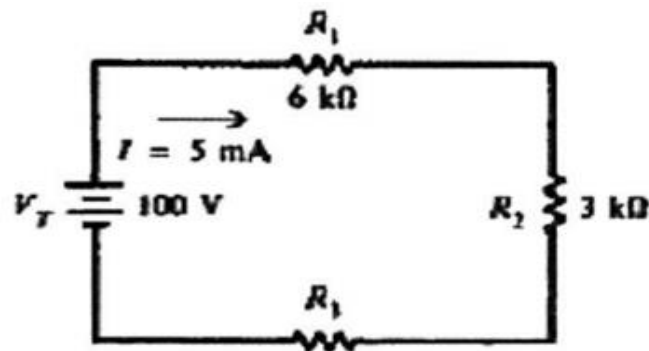- 1- As shown in figure below, calculate the value of resistance R_3 and the voltages of each resistances **using voltage divider's law**. (answer: $R_3=11K \Omega$, $V_1=30v$, $V_2=15v$, $v=55v$)




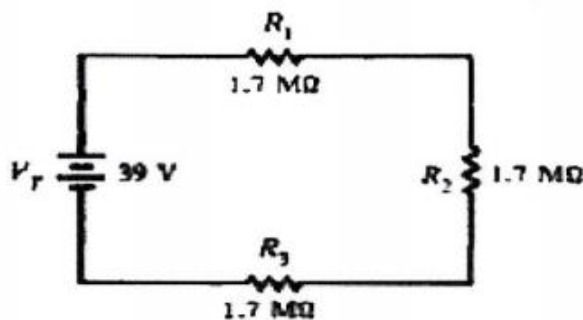- 2- As shown in figure below , calculate total current and the voltages of each resistances **using voltage divider's law**. (answer: $I=7.65\mu A$, $V_1=13v$, $V_2=13v$, $V_3=13v$)




3- for the circuit shown in figure below, calculate:

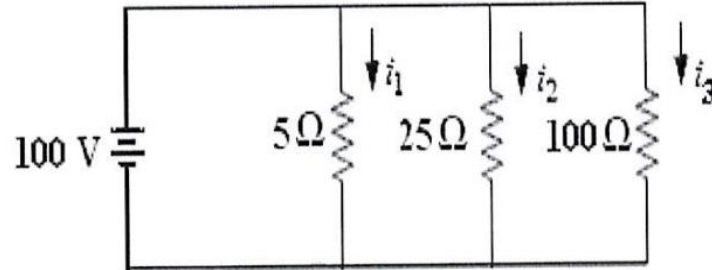- 1) equivalent resistance
- 2) currents of each resistance (i_1 , i_2 , and i_3)
- 3) total current



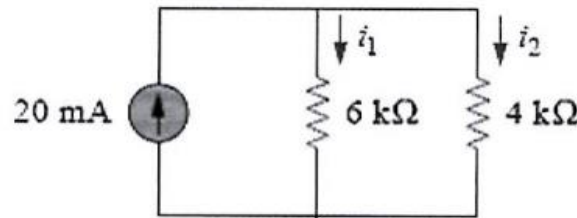
4-for the circuit shown in figure below, calculate the currents of each resistance (i_1 , i_2) **using current divider's law**.



رقم المحاضرة: الخامسة	Series and Parallel Circuits
عنوان المحاضرة:	سماء خالد غانم
اسم المدرس:	المرحلة أولى\الفصل الدراسي الأول\ قسم التقنيات الإلكترونية\المعهد التقني الموصل
الفئة المستهدفة :	ان يتعرف الطالب على ربط التوالي -التوازي في الدوائر الكهربائية
الهدف العام من المحاضرة :	1-ان يكون الطالب قادرا على التميز ان الربط هو توالي -توازي في الدوائر الكهربائية 2-ان يكون الطالب قادرا على إيجاد المقاومة المكافئة و التيار و الفولتية لكل مقاومة في الدائرة الكهربائية ذات الربط توالي- توازي.
الأهداف السلوكية او مخرجات التعلم:	1.القاء المحاضرة 2.التعليم المدمج 3.المناقشة 4.التقارير
استراتيجيات التيسير المستخدمة	سيكون الطالب قادرا على إيجاد المقاومة المكافئة وكلا من الفولتية و التيار لكل مقاومة في ربط التوالي – التوازي في الدائرة الكهربائية
المهارات المكتسبة	امتحانات يومية-امتحانات شهرية
طرق القياس المعتمدة	

الاسئلة القبلية

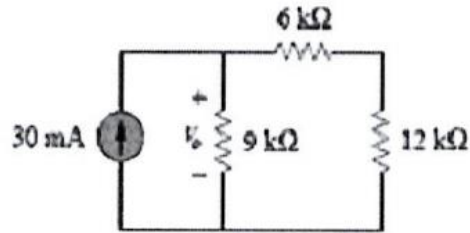Determine the combination in the circuit as shown figure below



المحتوى العلمي

- Series -parallel combination
- Examples


محتويات المحاضرة

Series -parallel combination




In the Series -parallel combination circuit, the circuit components are series connected in same part and parallel in other part. We won't be able to apply a single set of the rules to every of the circuit. Instead, we will have to identify which parts of the circuit are series and which parts are parallel, then selectivity applies series and parallel rules as necessary to determine what is happening.

Example: For the circuit shown in figure below , determine:

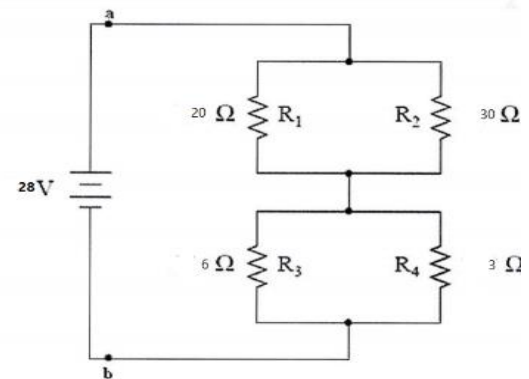- 1) The total current
- 2) The voltage and currents of each resistance



Solution: 1)

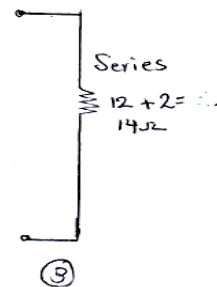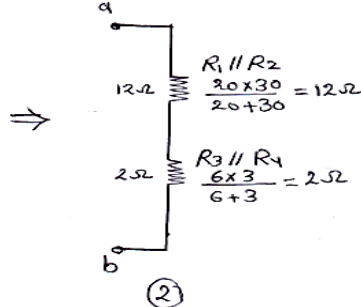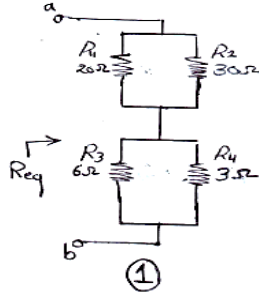

$$\therefore R_{eq} = 14\Omega$$

$$I = \frac{V}{R_{eq}} = \frac{28}{14} = 2A$$

2) Current-divider's law:-

$$I_1 = \frac{2}{20+30} * 30 = 1.2$$

$$I_2 = \frac{2}{20+30} * 20 = 0.8A$$

$$V_1 = I_1 * R_1 = 1.2 * 20 = 24V$$

$$V_2 = I_2 * R_2 = 0.8 * 30 = 24V$$

$$V_1 = V_2 = 24V \text{ [because } R_1 \text{ and } R_2 \text{ is parallel]}$$


$$I_3 = \frac{2}{6+3} * 3 = 0.667A$$

$$I_4 = \frac{2}{6+3} * 6 = 1.333$$


$$\therefore V_3 = I_3 * R_3 = 0.667 * 6 = 4V$$

$$V_4 = I_4 * R_4 = 1.333 * 3 = 4V$$

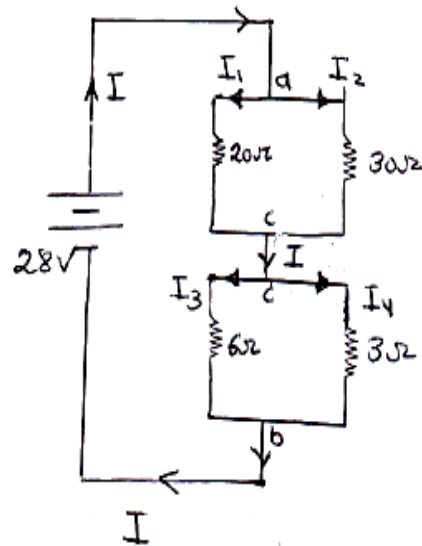
$$V_3 = V_4 = 4V \text{ [because } R_3 \text{ and } R_4 \text{ is parallel]}$$



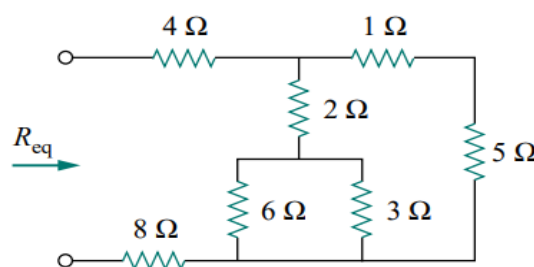
Example: Find the equivalent resistance of the circuit shown in figure below.




Solution:

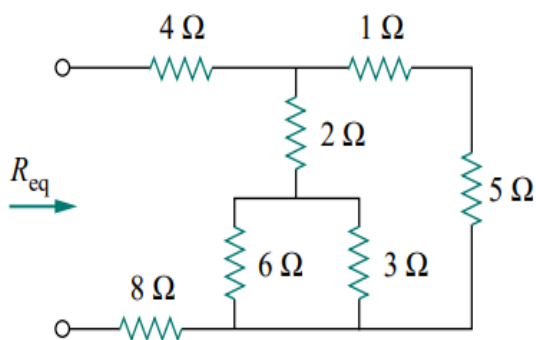


(1)

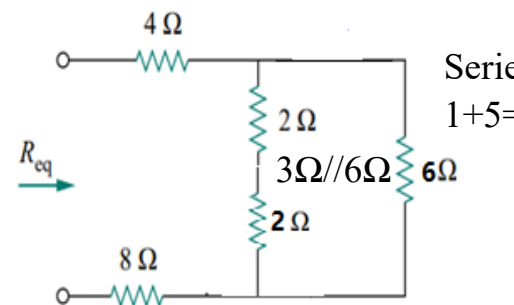


(2)

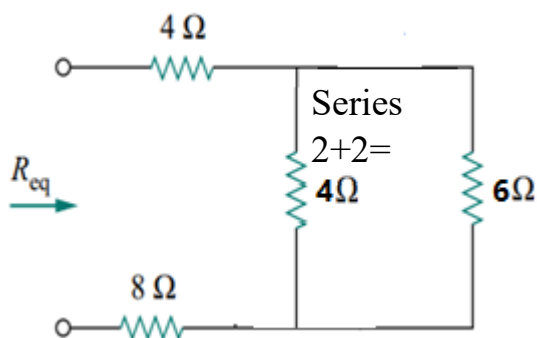

(3)

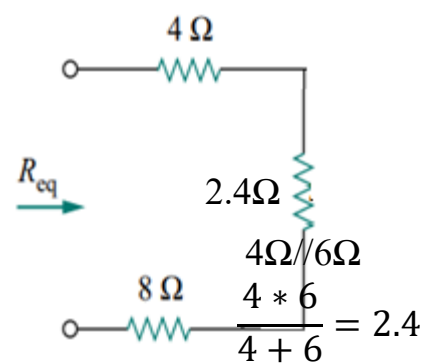

(4)

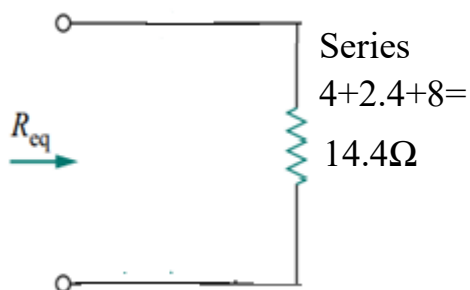


(5)


$$R_{eq} = 14.4\Omega$$

Example: For the circuit shown in figure below, Find:

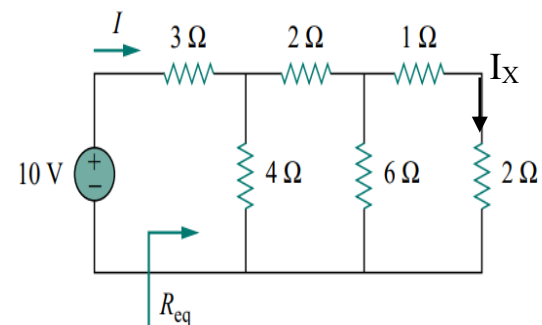- 1) The total current I .
- 2) The value of I_x .



Solution:

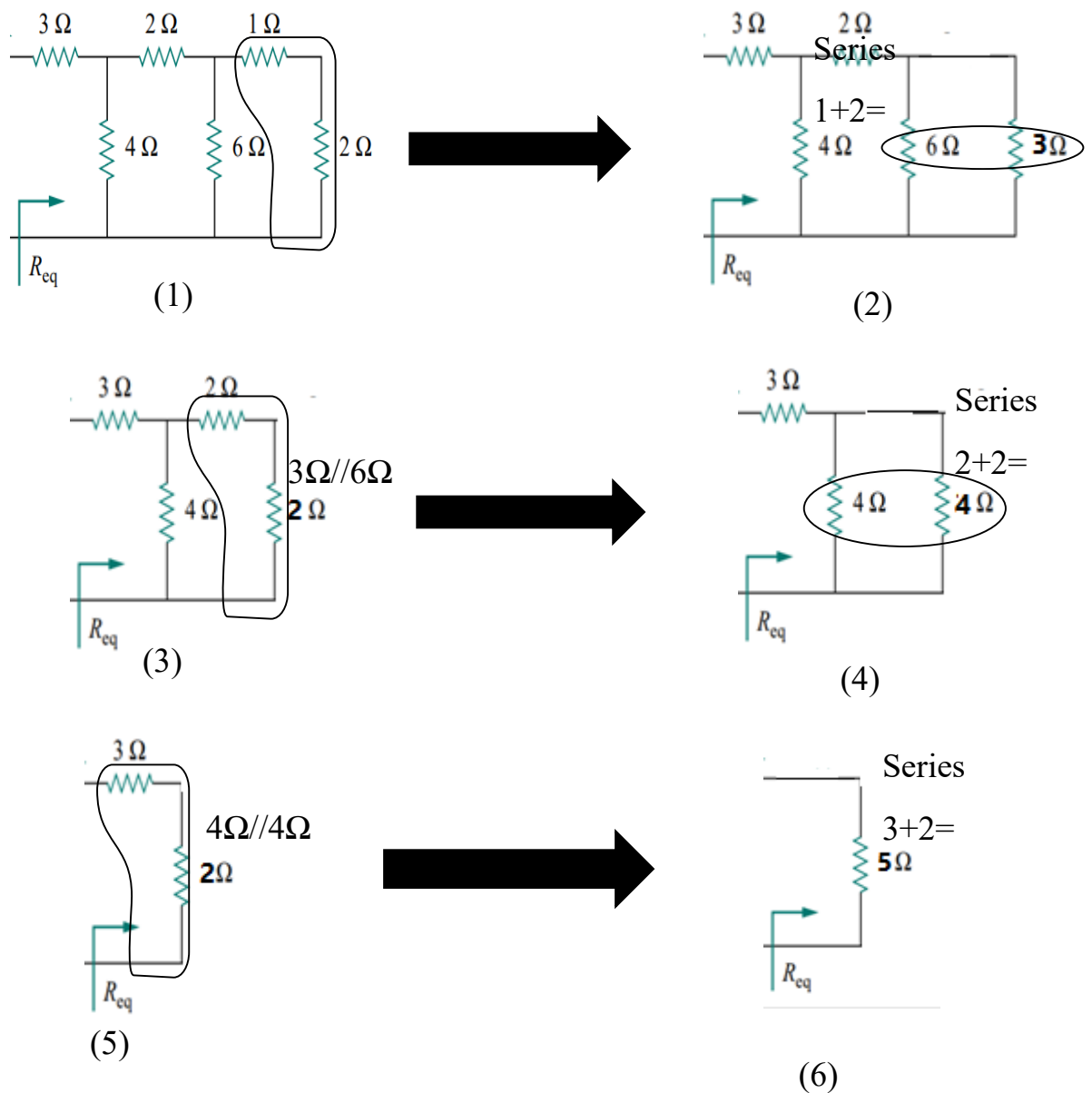



$$R_{eq} = 5\Omega$$

$$I = \frac{10}{5} = 2A$$

2) by using current divider's law


From figure (4) can be given I_1 :

$$I_1 = \frac{2}{4+4} * 4 = 1A$$

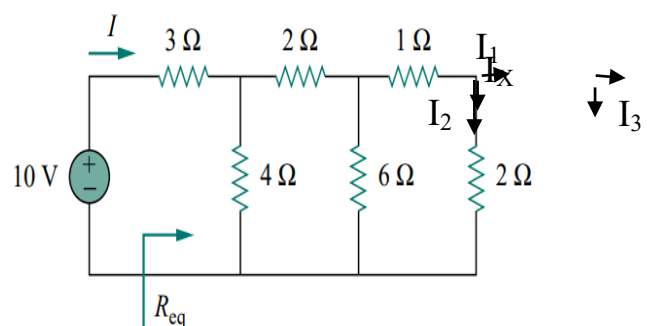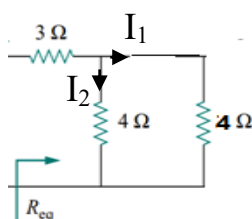

$$I_x = \frac{1}{6+3} * 6 = 0.667A$$

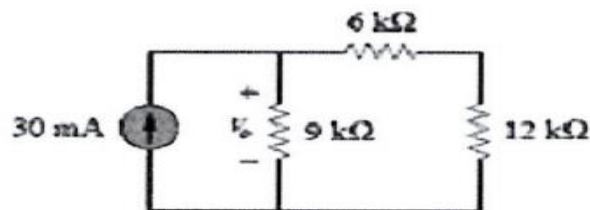Example: For the circuit shown in figure below, Find the value of V_0 (the voltage of $9K\Omega$)



Solution:

$6K\Omega$ and $12K\Omega$ is series

$$6K + 12K = 18K\Omega$$


Can be using current divider's law

$$I_0 = \frac{30 * 10^{-3}}{(9 * 10^3 + 18 * 10^3)} * (18 * 10^3) = 0.02A$$

$$V_0 = I_0 * R_{9K\Omega}$$


$$V_0 = 0.02 * 9 * 10^3$$

$$V_0 = 180V$$

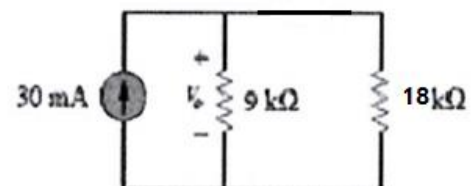


الأسئلة البعدية

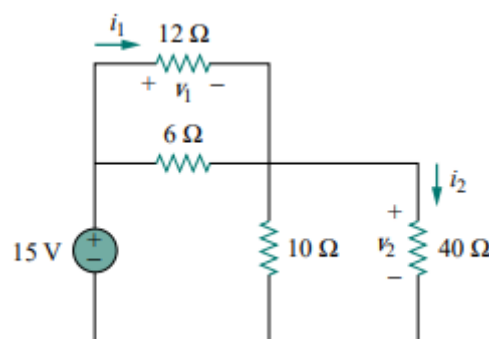
- 1- Find i_1 and i_2 in the circuit shown in Figure below. Also calculate v_1 and v_2 . (Answer: $v_1 = 5V$, $i_1 = 0.416A$, $v_2 = 10V$, $i_2 = 0.250A$.)



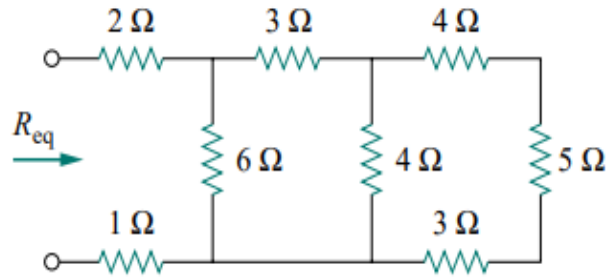- 2- Find equivalent resistance in the circuit shown in Figure below. (Answer: $R_{eq}=6\Omega$.)



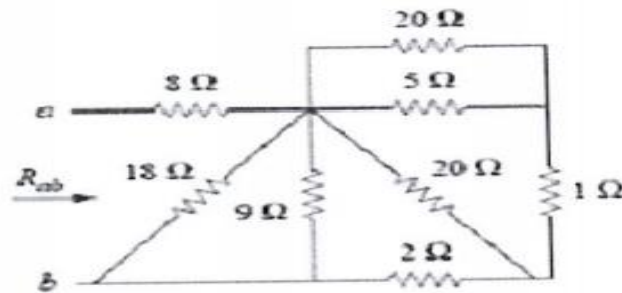- 3- Find equivalent resistance in the circuit shown in Figure below. (Answer: $R_{ab}=11\Omega$.)



رقم المحاضرة: السادسة	عنوان المحاضرة: star-delta transformations
اسم المدرس: سماء خالد غانم	المرحلة الأولى الفصل الدراسي الأول قسم التقنيات الإلكترونية المعهد التقني الموصل
الهدف العام من المحاضرة :	1- ان يتعرف الطالب على ربط دلتا- نجمة في الدوائر الكهربائية
الأهداف السلوكية او مخرجات التعلم:	1- ان يكون الطالب قادرا على التميز بين ربط النجمي و ربط الدلتا في الدوائر الكهربائية 2- ان يكون الطالب قادرا على تحويل دلتا الى نجمة والعكس و إيجاد المقاومة المكافئة .
استراتيجيات التيسير المستخدمة	1. القاء المحاضرة 2. التعليم المدمج 3. المناقشة 4. التقارير
المهارات المكتسبة	سيكون الطالب قادرا على تحويل دلتا الى نجمة والعكس و إيجاد المقاومة المكافئة وكلا من الفولطية و التيار لكل مقاومة في الدائرة الكهربائية
طرق القياس المعتمدة	امتحانات يومية- امتحانات شهرية

الاسئلة القبلية

-Why used delta -star transformations?


المحتوى العلمي

- Wye-delta transformations
- Examples


محتويات المحاضرة

Wye-delta transformations

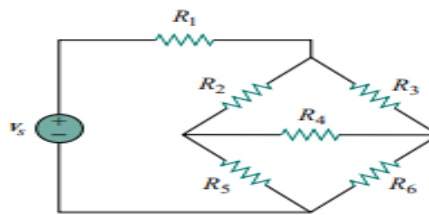
There are some cases often a rise in circuit analysis, when resistors are neither in parallel nor in series. For example, consider the circuit shown in figure below



Star (wye or T) connection:

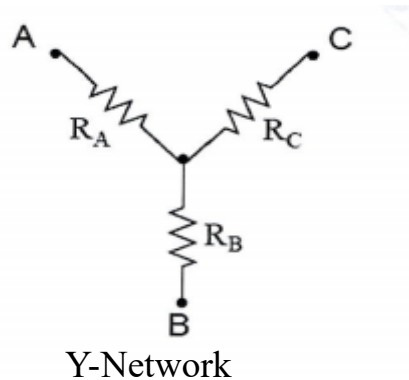


Y-Network

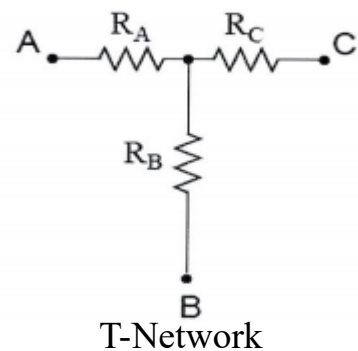


T-Network

Delta (Δ or π) connection:

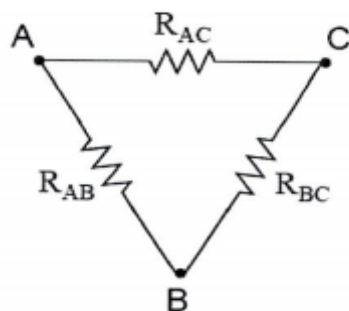

Δ -Network

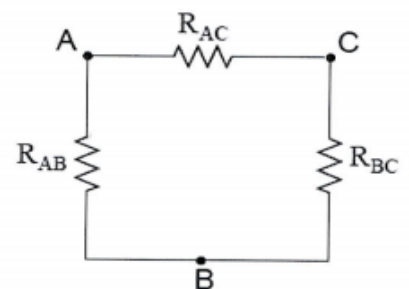


π Network

To convert a Delta (Δ) to Wye (Y):

$$R_A = \frac{R_{AB} R_{AC}}{R_{AB} + R_{AC} + R_{BC}}$$

$$R_B = \frac{R_{AB} R_{BC}}{R_{AB} + R_{AC} + R_{BC}}$$
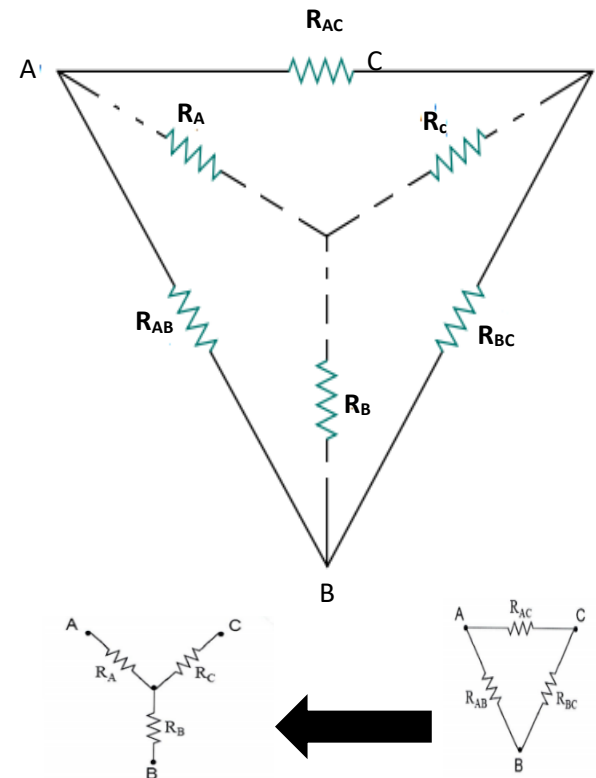
$$R_C = \frac{R_{AC} R_{BC}}{R_{AB} + R_{AC} + R_{BC}}$$




4.1.2 To convert a Wye (Y) to Delta (Δ):


$$R_{AB} = R_A + R_B + \frac{R_A R_B}{R_C}$$

$$R_{BC} = R_B + R_C + \frac{R_B R_C}{R_A}$$


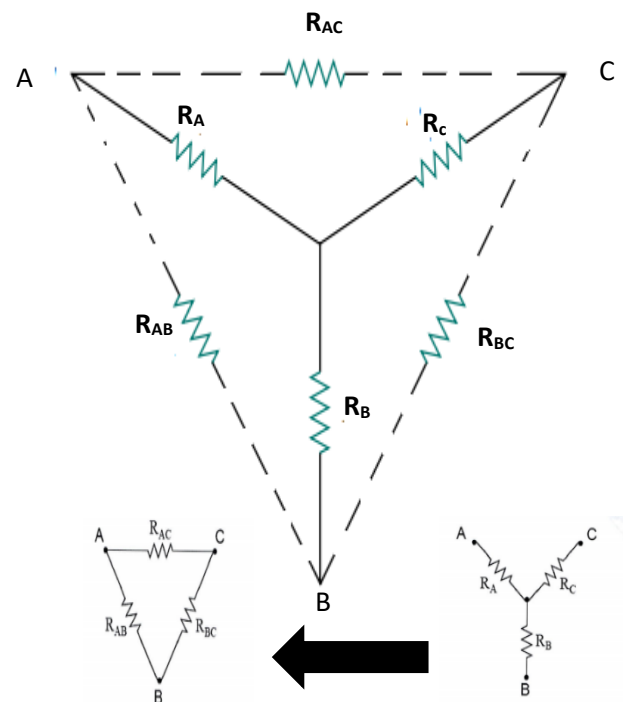
$$R_{AC} = R_A + R_C + \frac{R_A R_C}{R_B}$$



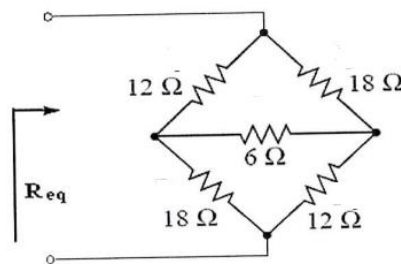Example: Using (Δ -Y) transformations to find the equivalent resistance and total current of the circuit shown in figure below (let voltage source $V = 10\text{V}$).



Solution:

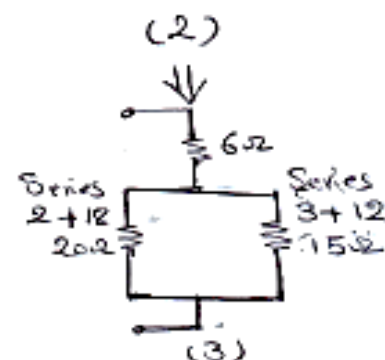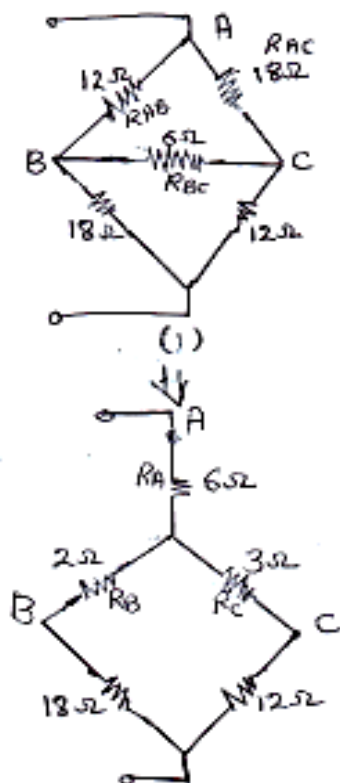

transform $\Delta \rightarrow Y$
 $\therefore R_{AB} = 12\Omega$, $R_{AC} = 18\Omega$, $R_{BC} = 6\Omega$

$$R_A = \frac{R_{AB} R_{AC}}{R_{AB} + R_{AC} + R_{BC}}$$

$$= \frac{12 \times 18}{12 + 18 + 6} = \frac{216}{36} = 6\Omega$$

$$R_B = \frac{R_{AB} R_{BC}}{R_{AB} + R_{AC} + R_{BC}}$$


$$= \frac{12 \times 6}{12 + 18 + 6} = \frac{72}{36} = 2\Omega$$

$$R_C = \frac{R_{AC} R_{BC}}{R_{AB} + R_{AC} + R_{BC}}$$


$$= \frac{18 \times 6}{12 + 18 + 6} = \frac{108}{36} = 3\Omega$$

$\Rightarrow$

28

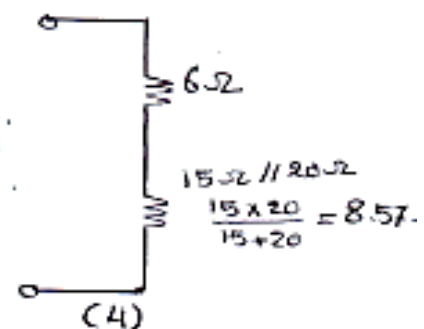

$$\therefore R_{eq} = 14.57 \Omega$$

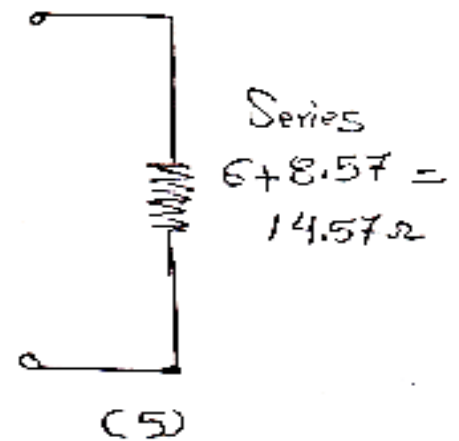


➤ Total current (Voltage source (10v))


$$I = \frac{V}{R_{eq}}$$

$$I = \frac{10}{14.57}$$

$$I = 0.686 \text{ A}$$

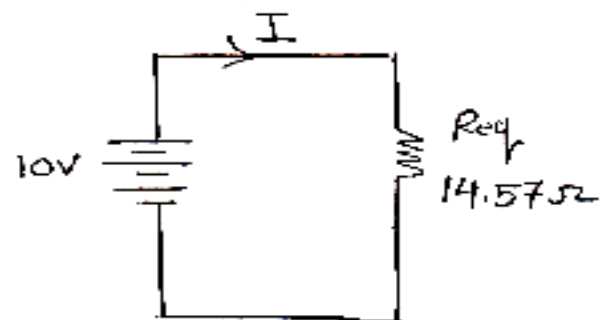

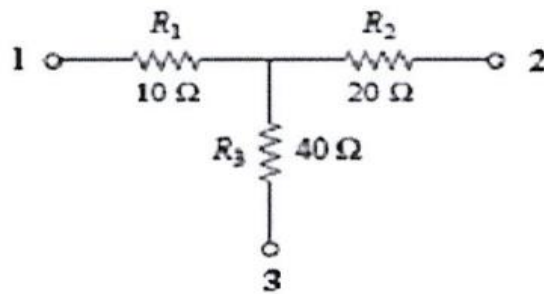Example: Convert a Wye (Y) Network to equivalent Delta (Δ) Network for the circuit shown in figure below.



Solution:


transform $Y \rightarrow \Delta$:-

$$R_1 = 10\Omega, R_2 = 20\Omega, R_3 = 40\Omega$$


$$\begin{aligned} R_{12} &= R_1 + R_2 + \frac{R_1 R_2}{R_3} \\ &= 10 + 20 + \frac{10 \times 20}{40} \\ &= 35\Omega \end{aligned}$$

$$\begin{aligned} R_{23} &= R_2 + R_3 + \frac{R_2 R_3}{R_1} \\ &= 20 + 40 + \frac{20 \times 40}{10} \\ &= 140\Omega \end{aligned}$$
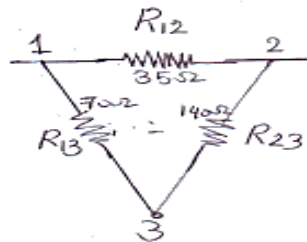
$$\begin{aligned} R_{13} &= R_1 + R_3 + \frac{R_1 R_3}{R_2} \\ &= 10 + 40 + \frac{10 \times 40}{20} \\ &= 70\Omega \end{aligned}$$




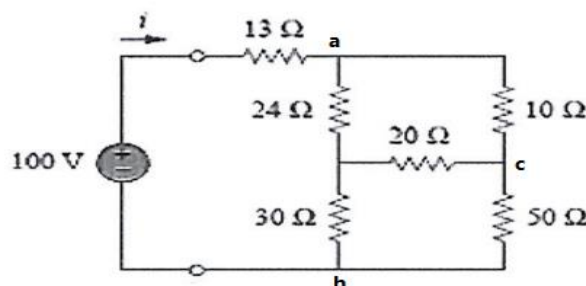Example: Find the equivalent resistance and total current of the circuit shown in figure below by Using (Y- Δ) transformations of the nodes a, b and c.




Solution:


Solution:

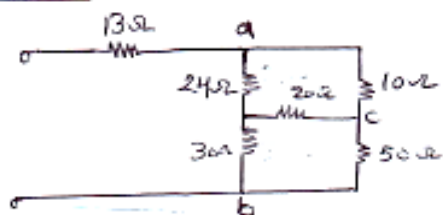

(1)

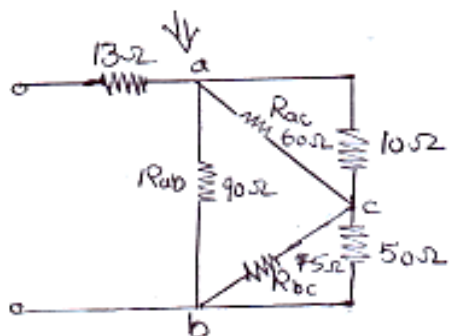

(2)

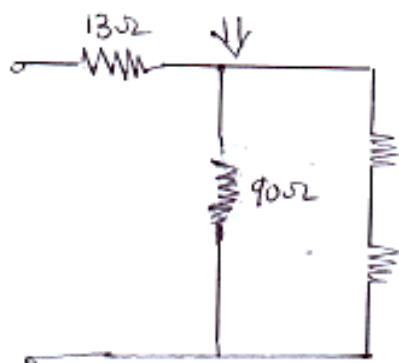

(3)

transform $T \rightarrow \Delta$

$$R_a = 24\Omega, R_b = 30\Omega, R_c = 20\Omega$$


$$R_{ab} = R_a + R_b + \frac{R_a R_b}{R_c} = 24 + 30 + \frac{24 \times 30}{20} = 90\Omega$$

$$R_{bc} = R_b + R_c + \frac{R_b R_c}{R_a} = 30 + 20 + \frac{30 \times 20}{24} = 75\Omega$$

$$R_{ac} = R_a + R_c + \frac{R_a R_c}{R_b} = 24 + 20 + \frac{24 \times 20}{30} = 60\Omega$$


$$10\Omega // 60\Omega = \frac{10 \times 60}{10 + 60} = 8.57\Omega$$
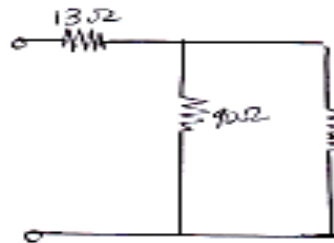
$$50\Omega // 75\Omega = \frac{50 \times 75}{50 + 75} = 30\Omega$$



Series
 $8.57 + 30$
 38.57Ω

(4)

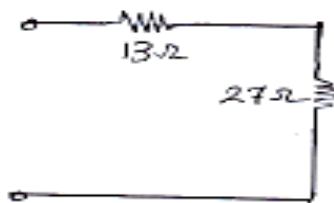

$$38.57\Omega // 90\Omega = \frac{38.57 \times 90}{38.57 + 90} = 27\Omega$$

(5)




Series
 $(13 + 27)$
 40Ω

(6)


$$I = \frac{V}{R_{eq}}$$

$$I = \frac{100}{40} = 2.5A$$

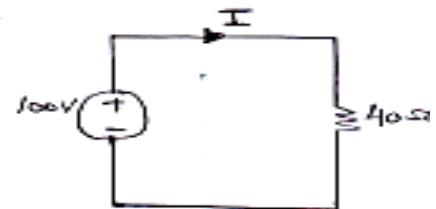


الأسئلة البعيدة

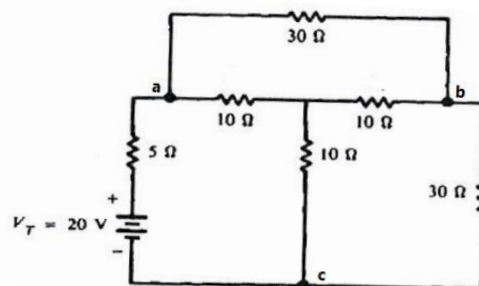- Find the equivalent resistance and total current of the circuit shown in figure below by **Using (Y-Δ) transformation** of the nodes a, b and c. (answer: 20Ω)



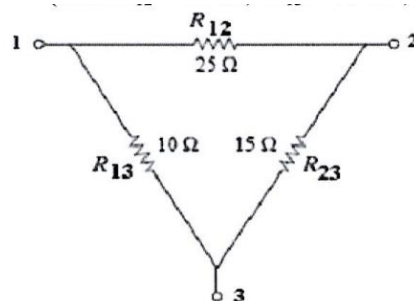2- Convert Delta (Δ) Network a to equivalent Wye (Y) Network for the circuit shown in figure below.



رقم المحاضرة: الثامنة	
عنوان المحاضرة:	Kirchhoff's law
اسم المدرس:	سماء خالد غانم
الفئة المستهدفة :	المرحلة أولى\الفصل الدراسي الأول\ قسم التقنيات الإلكترونية\المعهد التقني الموصل
الهدف العام من المحاضرة :	ان يفهم الطالب قانون كيرشوف
الأهداف السلوكية او مخرجات التعلم:	1- ان يكون الطالب قادرا على تطبيق وتحليل الدائرة باستخدام قانون كيرشوف 2- ان يكون الطالب قادرا على ايجاد التيار والفولتية لكل مقاومة في الدائرة باستخدام قانون كيرشوف .
استراتيجيات التيسير المستخدمة	1. القاء المحاضرة 2. التعليم المدمج 3. المناقشة 4. التقارير
المهارات المكتسبة	1- سيتمكن الطالب من تحليل الدائرة الكهربائية التي يصعب حلها باستخدام قانون اوم 2- سيكون الطالب قادرا على تطبيق قانون كيرشوف و إيجاد كلا من الفولتية والتيار لكل مقاومة في الدائرة الكهربائية.
طرق القياس المعتمدة	امتحانات يومية-امتحانات شهرية الاسئلة القبليّة

-define: node, loop, branch

المحتوى العلمي

- Kirchhoff's law method (Branch current method)
- Examples


محتويات المحاضرة

Kirchhoff's law method (Branch current method)


In This method, we assume direction of the current in network, then write equations describing their relationships to each other through Kirchhoff's and ohm's laws. Once we have one equation for every unknown current, we can

solve the simultaneous equation and determine all the current and therefore all voltage drops in the network.

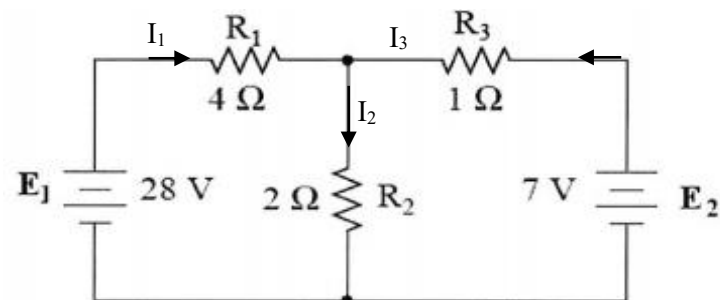Example : from the circuit shown in figure below find all the currents in the resistance by using Kirchhoff's law method.



Solution:

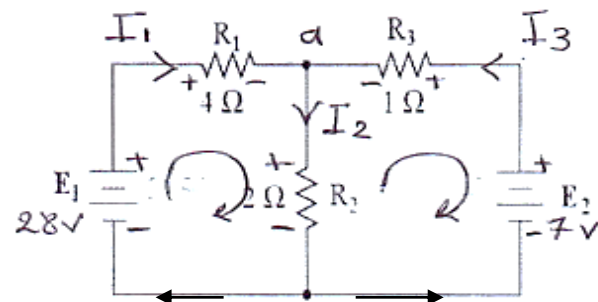

KCL at node (a)

$$I_1 - I_2 + I_3 = 0$$

$$\therefore I_1 = I_2 - I_3 \quad \text{----- (1)}$$

KVL for Loop (1):

$$-28 + 4I_1 + 2I_2 = 0$$

$$4I_1 + 2I_2 = 28 \quad \text{----- (2)}$$

KVL For Loop (2)

$$-2 I_2 - I_3 + 7 = 0$$

$$-2 I_2 - I_3 = -7 \quad \text{---- (3)}$$

نعوض المعادلة رقم (1) في المعادلة رقم (3)

$$4 I_1 - 2 I_2 = 28$$

$$4 (I_2 - I_3) + 2 I_2 = 28$$

$$4 I_2 - 4 I_3 + 2 I_2 = 28$$

$$6 I_2 - 4 I_3 = 28 \quad \text{---- (4)}$$

نجمع معادلة رقم (3) مع معادلة رقم (4) ونعيد الجداول

$$[-2 I_2 - I_3 = -7] \times 3 \quad \text{---- (3)}$$

$$6 I_2 - 4 I_3 = 28 \quad \text{---- (4)}$$

$$\hline -6 I_2 - 3 I_3 = -21 \quad \text{---- (3)}$$

$$6 I_2 - 4 I_3 = 28 \quad \text{---- (4)}$$

$$\hline -7 I_3 = 7$$

$$\therefore \underline{\underline{I_3 = -1 A}}$$

نعوض I_3 في المعادلة رقم (2) أو (4) لإيجاد I_2

$$-2 I_2 - I_3 = -7 \quad \text{---- (3)}$$


$$-2 I_2 - (-1) = -7 \Rightarrow -2 I_2 = -7 - 1$$

$$-2 I_2 = -8$$

$$\therefore \underline{\underline{I_2 = \frac{-8}{-2} = 4 A}}$$

$$\underline{\underline{I_1}} = I_2 - I_3 \Rightarrow I_1 = 4 - (-1) = \underline{\underline{5 A}}$$

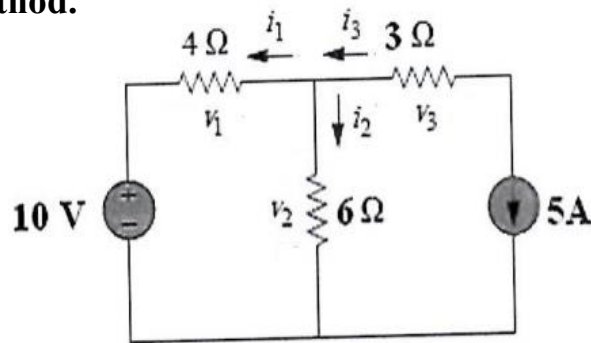Example: Find the voltage of resistances to the circuit shown in figure below using Branch current method.



Solution:

هناك مصدر التيار في احد اطراف الدائرة اي ان احد تيارات معلوم وهو i_3

$i_3 = -5$ لان الاتجاه المفروض عكس اتجاه المصدر

KCL at node a

$$-i_1 - i_2 + i_3 = 0$$

$$i_1 = -i_2 + i_3$$

$$i_1 = -i_2 - 5 \quad \dots\dots\dots (1)$$

KCL at node a

$$-10 - 4i_1 + 6i_2 = 0 \quad \dots\dots\dots (2)$$

نعوض المعادلة (1) في معادلة (2)

$$-10 - 4(-i_2 - 5) + 6i_2 = 0$$

$$-10 + 4i_2 + 20 + 6i_2 = 0 \quad \Longrightarrow \quad 10 + 10i_2 = 0 \quad \Longrightarrow \quad i_2 = -10/10 \quad \Longrightarrow \quad i_2 = -1 \text{ A}$$


نعوض i_2 في معادلة (1)

$$i_1 = -i_2 - 5 \quad \Longrightarrow \quad i_1 = -(-1) - 5 \quad \Longrightarrow \quad i_1 = -4 \text{ A}$$

$$V_1 = i_1 * R_{4\Omega} = -4 * 4 = -16 \text{ V}$$

$$V_2 = i_2 * R_{6\Omega} = -1 * 6 = -6 \text{ V}$$
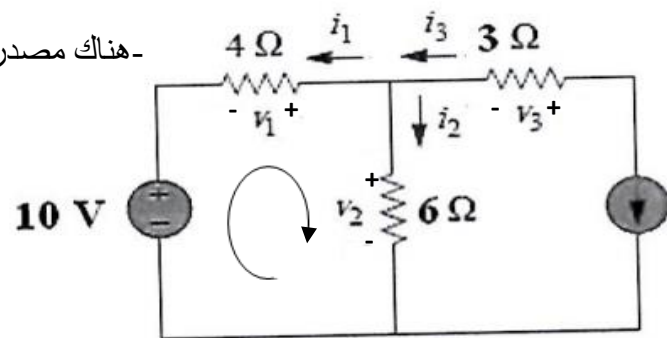
$$V_3 = i_3 * R_{3\Omega} = -5 * 3 = -15 \text{ V}$$



Example: Find the voltage of resistances to the circuit shown in figure below using Branch current method.

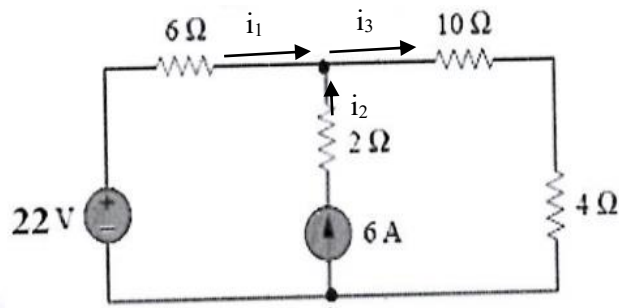


Figure (5.3)

Solution:

-هناك مصدر التيار في وسط ال loops اي ان احد تيارات معلوم وهو i_2


$$i_2 = 6A$$

KCL at node a

$$i_1 + i_2 - i_3 = 0$$

$$i_1 = -i_2 + i_3$$
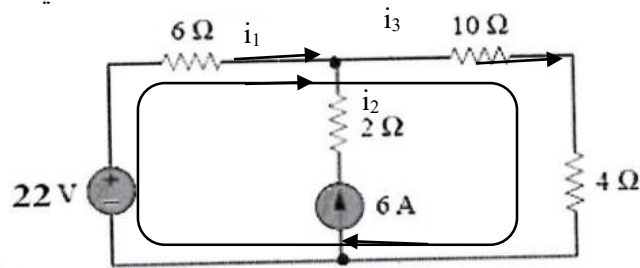
$$i_1 = -6 + i_3 \quad \dots\dots\dots (1)$$



KVL for super loop

$$-22 + 6i_1 + 10i_3 + 4i_3 = 0$$

$$-22 + 6i_1 + 14i_3 = 0 \quad \dots\dots\dots (2)$$

نعوض المعادلة (1) في معادلة (2)

$$-22 + 6(-6 + i_3) + 14i_3 = 0$$

$$-22 + (-6*6) + 6i_3 + 14i_3 = 0 \implies -22 - 36 + 20i_3 = 0 \implies i_3 = -58 / -20 \implies$$

$$i_3 = 2.9A$$

نعوض i_3 في معادلة (1)

$$i_1 = -6 + i_3 \implies i_1 = -6 + (2.9) \implies i_1 = -3.1A$$

$$V_{6\Omega} = i_1 * R_{6\Omega} = -3.1 * 6 = -18.6$$


$$V_{2\Omega} = i_2 * R_{2\Omega} = 6 * 2 = 12v$$

$$V_{4\Omega} = i_3 * R_{4\Omega} = 2.9 * 4 = 11.6v$$


$$V_{10\Omega} = i_3 * R_{10\Omega} = 2.9 * 10 = 29v$$

الأسئلة البعدية

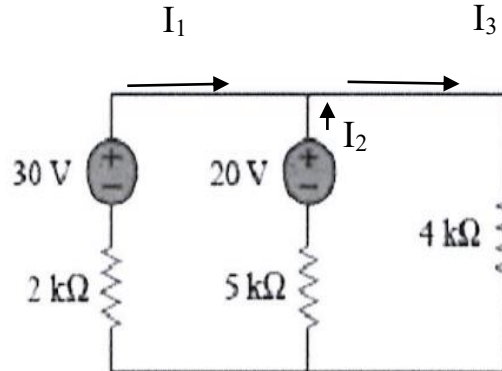
- 1- From the circuit shown in figure below find all the currents in the resistance by using Kirchhoff's law method. (answer: $I_1=5\text{mA}$, $I_2=0\text{A}$, $I_3=5\text{mA}$)



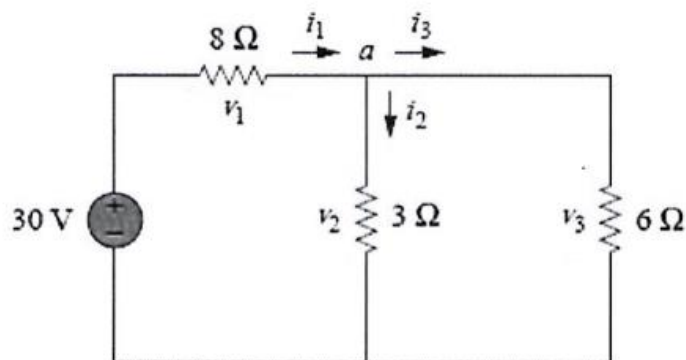- 2- From the circuit shown in figure below, find the v_1 , v_2 and v_3 of the resistance by using Kirchhoff's law method. (answer: $i_1=3\text{A}$, $i_2=2\text{A}$, $i_3=1\text{A}$)



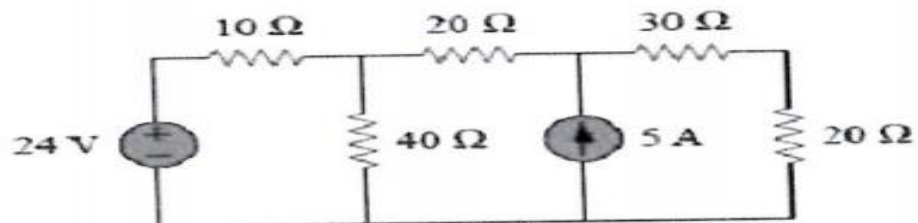- 3- From the circuit shown in figure below, find the main equations only by using Kirchhoff's law method.



رقم المحاضرة :التاسعة	
عنوان المحاضرة:	Mesh method
اسم المدرس:	سماء خالد غانم
الفئة المستهدفة :	المرحلة أولى\الفصل الدراسي الأول\ قسم التقنيات الإلكترونية\المعهد التقني الموصل
الهدف العام من المحاضرة :	ان يفهم الطالب كيفية تحليل وتطبيق طريقة Mesh في الدائرة الكهربائية
الأهداف السلوكية او مخرجات التعلم:	1-ان يكون الطالب قادرا على تطبيق وتحليل الدائرة باستخدام طريقة Mesh 2-ان يكون الطالب قادرا على ايجاد التيار والفولتية لكل مقاومة في الدائرة باستخدام طريقة Mesh
استراتيجيات التيسير المستخدمة	1. القاء المحاضرة 2. التعليم المدمج 3. المناقشة 4. التقارير
المهارات المكتسبة	3- سيتمكن الطالب من تحليل الدائرة الكهربائية التي يصعب حلها باستخدام قانون اوم 4- سيكون الطالب قادرا على تطبيق وحل الدائرة الكهربائية بطريقة Mesh و إيجاد كلا من الفولتية و التيار لكل مقاومة في الدائرة الكهربائية.
طرق القياس المعتمدة	امتحانات يومية-امتحانات شهرية

الاسئلة القبلية

-Define KCL, KVL.

المحتوى العلمي


- Mesh method (Maxwell current loop method)
- Examples

محتويات المحاضرة

Mesh method (Maxwell current loop method)

Mesh analysis provides another general procedure for analyzing circuits, using mesh currents as the circuit variables. Using mesh currents instead of element currents as circuit variables is convenient and reduces the number of equations that must be solved simultaneously. Recall that a loop is a closed path with no node passed more than once. A mesh is a loop that does not contain any other loop within it. Mesh analysis is also known as loop analysis or the mesh-current method. Mesh method applies KVL only to find unknown voltages or current in a given circuit, while KCL not applies.

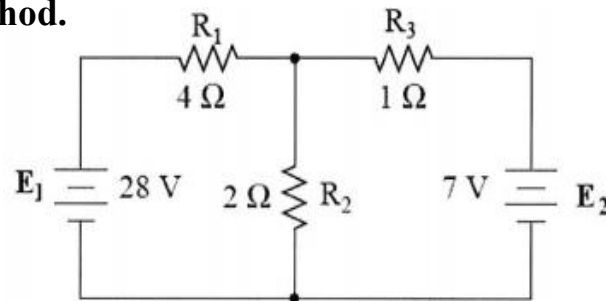Example : From the circuit shown in figure below, find all the currents in the resistance by using Mesh method.




Solution:

Mesh (1) KVL :-

$$-28 + 4I_1 + 2(I_1 - I_2) = 0$$

$$-28 + 4I_1 + 2I_1 - 2I_2 = 0$$
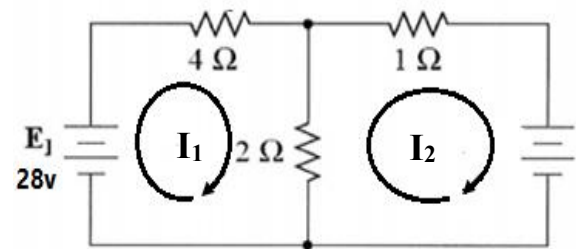
$$\therefore 6I_1 - 2I_2 = 28 \quad \text{--- (1)}$$



Loop (2) KVL :-

$$2(I_2 - I_1) + I_2 + 7 = 0$$

$$2I_2 - 2I_1 + I_2 + 7 = 0$$

$$\therefore 3I_2 - 2I_1 = -7 \quad \text{--- (2)}$$

$$\begin{array}{rcl}
 6I_1 - 2I_2 & = & 28 \quad \text{--- (1)} \\
 [-2I_1 + 3I_2 = -7] \times 3 & & \text{--- (2)} \\
 \hline
 \cancel{6I_1} - 2I_2 & = & 28 \quad \text{--- (1)} \\
 \cancel{-6I_1} + 9I_2 & = & -21 \quad \text{--- (2)} \\
 \hline
 7I_2 & = & 7 \Rightarrow I_2 = 1A
 \end{array}$$

$$\therefore \boxed{I_2 = 1A = I_{R_3}}$$

$$6I_1 - 2I_2 = 28 \quad \text{--- (1)}$$

$$6I_1 - 2 \times 1 = 28 \Rightarrow 6I_1 = 28 + 2$$

$$\therefore I_1 = \frac{30}{6} = 5A$$


$$\boxed{I_1 = I_{R_1} = 5A}$$

$$I_{R_2} = I_{2R}$$


$$I_{R_2} = I_1 - I_2 = 5 - 1 = 4A$$

$$\therefore \boxed{I_{R_2} = 4A}$$

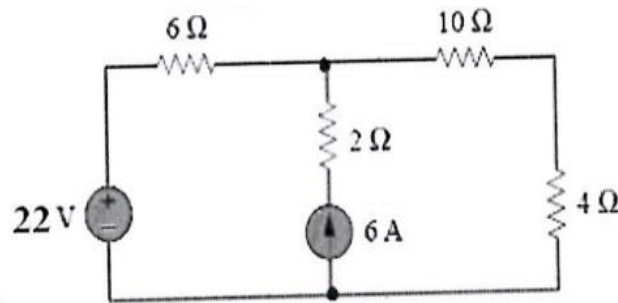Example : Find the voltage of resistances to the circuit shown in figure below using Maxwell current loop method.



Solution:

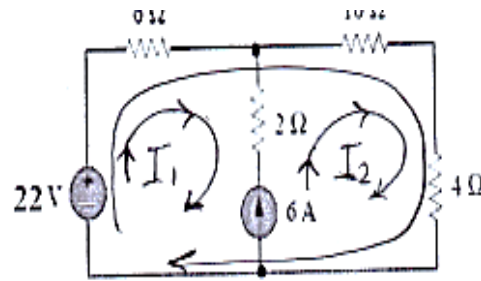

حجمر التيار في رسته ال (Loops) $I_2 - I_1 = 6A$

$$I_2 = 6 + I_1 \quad \text{--- (1)}$$

KVL supermesh

$$-22 + 6I_1 + 10I_2 + 4I_2 = 0$$

$$-22 + 6I_1 + 14I_2 = 0 \quad \text{--- (2)}$$

نحوه في معادله رقم (1) في معادله رقم (2)

$$-22 + 6I_1 + 14(6 + I_1) = 0$$

$$-22 + 6I_1 + 84 + 14I_1 = 0 \Rightarrow 62 = -20I_1 \Rightarrow$$

$$I_1 = -3.1A \quad \boxed{I_1 = I_{6\Omega} = -3.1A}$$

$$I_2 = 6 + I_1 \Rightarrow I_2 = 6 + (-3.1) = 2.9A$$

$$\boxed{I_2 = I_{10\Omega} = I_{4\Omega} = 2.9A}$$

$$\boxed{I_{2\Omega} = 6A}$$

41


$$V_{6\Omega} = I_1 * R_{6\Omega} = 3.1 * 6 = 18.6V$$

$$V_{2\Omega} = 6 * R_{2\Omega} = 6 * 2 = 12V$$


$$V_{10\Omega} = I_2 * R_{10\Omega} = 2.9 * 10 = 29V$$

$$V_{4\Omega} = I_2 * R_{4\Omega} = 2.9 * 4 = 11.6V$$

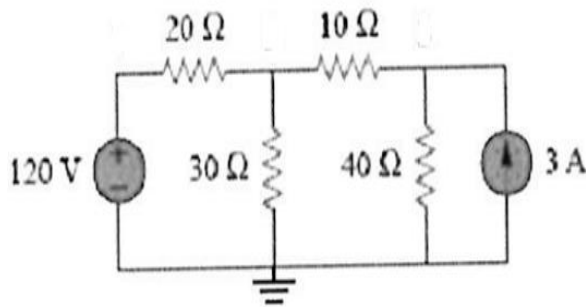Example: From the circuit shown in figure below find all the currents in the resistance by using Mesh method.



Solution:

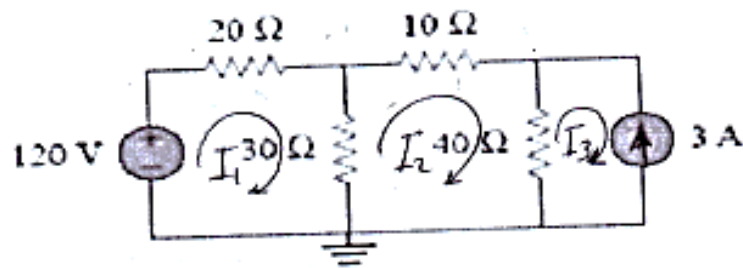

$$I_3 = -3A$$

Mesh (1) KVL

$$\begin{aligned} -120 + 20 I_1 + 30(I_1 - I_2) &= 0 \\ -120 + 50 I_1 - 30 I_2 &= 0 \\ 50 I_1 - 30 I_2 &= 120 \quad \text{--- (1)} \end{aligned}$$

Mesh (2) KVL

$$\begin{aligned} 30(I_2 - I_1) + 10 I_2 + 40(I_2 - I_3) &= 0 \\ 80 I_2 - 30 I_1 - 40 I_3 &= 0 \end{aligned}$$

$$80 I_2 - 30 I_1 - 40 (-3) = 0$$

$$80 I_2 - 30 I_1 = -120 \quad \text{--- (2)}$$

$$[50 I_1 - 30 I_2 = 120] * 8 \quad \text{--- (1)}$$

$$[-30 I_1 + 80 I_2 = -120] * 3 \quad \text{--- (2)}$$

$$400 I_1 - 240 I_2 = 960 \quad \text{--- (1)}$$

$$-90 I_1 + 240 I_2 = -360 \quad \text{--- (2)}$$

$$310 I_1 = 600$$

$$I_1 = 1.935 \text{ A}$$

$$I_1 = I_{20\Omega} = 1.935 \text{ A}$$

$$50 I_1 - 30 I_2 = 120 \quad \text{--- (1)}$$

$$50 * 1.935 - 30 I_2 = 120$$

$$I_2 = -0.775 \text{ A}$$

$$I_2 = I_{10\Omega} = -0.775 \text{ A}$$


$$I_{30\Omega} = I_1 - I_2 = 1.935 - (-0.775) = 2.71 \text{ A}$$

$$I_{40\Omega} = I_2 - I_3 = -0.775 - (-3) = 2.225 \text{ A}$$


الأسئلة البعدية

1-Find v_1 and v_2 of the circuit shown in figure below by using Mesh method.

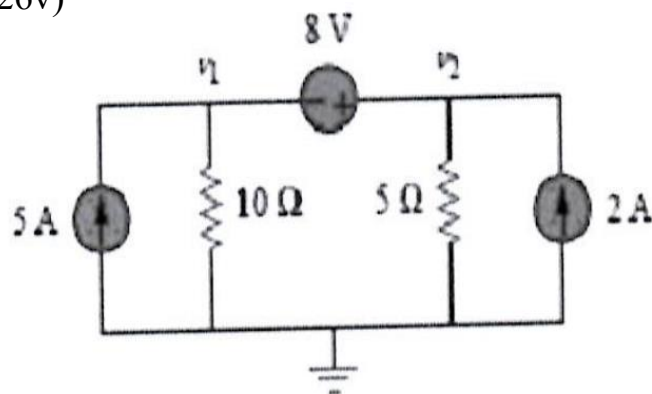(answer: $v_1 = 18 \text{ V}$, $v_2 = 26 \text{ V}$)



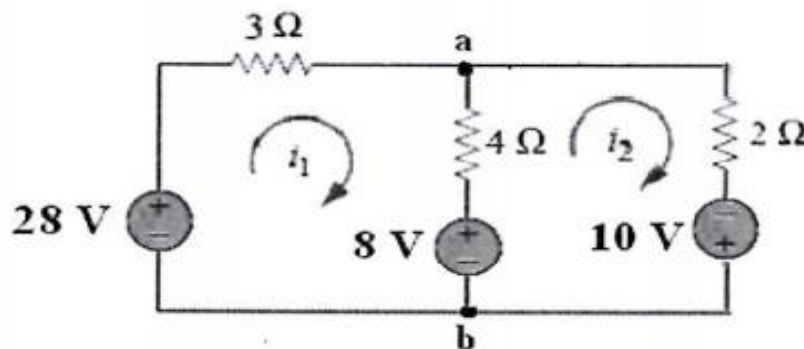2-Find v_1 and v_2 of the circuit shown in figure below by using Mesh method.
(answer: $i_1 = 6$ A, $i_2 = 7$ A)



رقم المحاضرة: التاسعة	عنوان المحاضرة:
Superposition theorem	اسم المدرس:
سماء خالد غانم	الفئة المستهدفة :
المرحلة أولى\الفصل الدراسي الأول\ قسم التقنيات الإلكترونية\المعهد التقني الموصل	الهدف العام من المحاضرة :
ان يفهم الطالب كيفية تحليل وتطبيق نظرية التراكمية في الدائرة الكهربائية	الأهداف السلوكية او مخرجات التعلم:
1-ان يكون الطالب قادرا على تطبيق وتحليل الدائرة باستخدام النظرية التراكمية 2-ان يكون الطالب قادرا على ايجاد التيار والفولتية لكل مقاومة في الدائرة باستخدام النظرية التراكمية	استراتيجيات التيسير المستخدمة
1.لقاء المحاضرة 2.التعليم المدمج 3.المناقشة 4.التقارير	المهارات المكتسبة
5- سيتمكن الطالب من تحليل الدائرة الكهربائية التي يصعب حلها باستخدام قانون اوم 6- سيكون الطالب قادرا على تطبيق وحل الدائرة الكهربائية باستخدام النظرية التراكمية و إيجاد كلا من الفولتية و التيار لكل مقاومة في الدائرة الكهربائية.	طرق القياس المعتمدة
امتحانات يومية-امتحانات شهرية	الاسئلة القبلية

-write the equations of current divider and voltage divider

المحتوى العلمي

- Superposition theorem:
- Examples

Superposition theorem:

The superposition principle states that the voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltages across (or currents through) that element due to each independent source acting alone.


The principle of superposition helps us to analyze a linear circuit with more than one independent source by calculating the contribution of each independent source separately. However, to apply the superposition principle.

We consider one independent source at a time while all other independent sources are turned off. This implies that we replace every voltage source by 0 V (or a short circuit), and every current source by 0 A (or an open circuit). This way we obtain a simpler and more manageable circuit. Other terms such as killed, made inactive, deadened, or set equal to zero are often used to convey the same idea.

Steps to Apply Superposition Principle:

1. Turn off all independent sources except one source. Find the output (voltage or current) due to that active source.
2. Repeat step 1 for each of the other independent sources.
3. Find the total contribution by adding algebraically all the contributions due to the independent sources

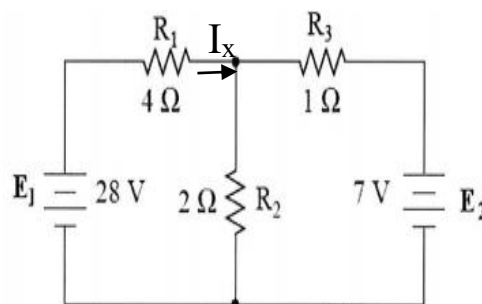Example: Use the superposition theorem to find I_x for 4Ω in the circuit in Figure below



Solution:

E₁ is On and E₂ is Off

E₂ is short circuit (because voltage source)

$$R'_{eq} = (1\Omega // 2\Omega) + 4\Omega$$

$$R'_{eq} = \left(\frac{1*2}{1+2}\right) + 4 = 0.667 + 4$$

=

$$4.667$$

$$I'_x = \frac{V}{R'_{eq}} = \frac{28}{4.667} = 6A$$

E₁ is Off and E₂ is On

E₁ is short circuit (because voltage source)

$$R''_{eq} = (4\Omega // 2\Omega) + 1\Omega$$

$$R''_{eq} = \left(\frac{4*2}{4+2}\right) + 1 = 0.332 + 1$$




$$= 1.332$$

$$I'' = \frac{V}{R'_{eq}} = \frac{7}{1.332} = 3A$$

$$I''_x = \frac{3}{4+2} * 2 = \frac{6}{6} = 1A \text{ (current divider's law)}$$

$$I_X = I'_x + I''_x = 6 - 1 = 5A$$

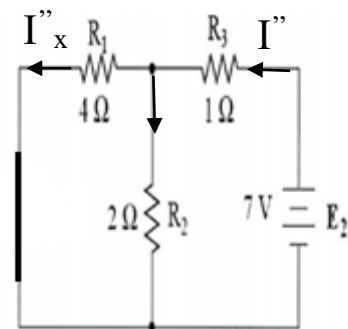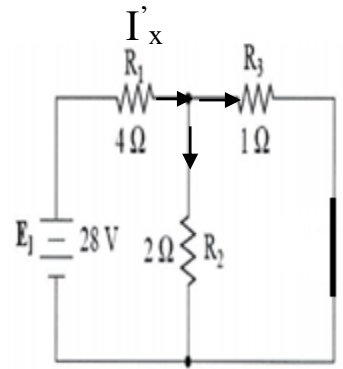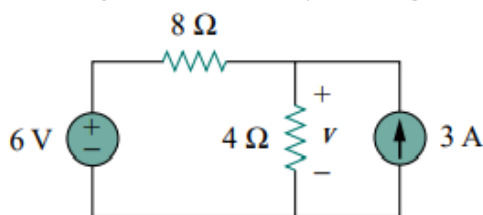Example: Find v in the circuit in Figure below by using the superposition theorem.




Solution:

6v is On and 3A is Off

3A is open circuit (because is current source)

$$I' = \frac{V}{R'_{eq}} = \frac{6}{8+4} = 0.5 \text{ A}$$

$$V' = 0.5 * 4 = 2V$$

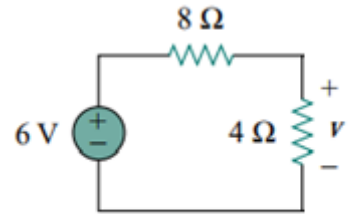


6v is Off and 3A is On

6v is short circuit (because is voltage source)

$$I'' = \frac{3}{8+4} * 8 = 2A \text{ (current divider's law)}$$


$$V'' = 2 * 4 = 8V$$

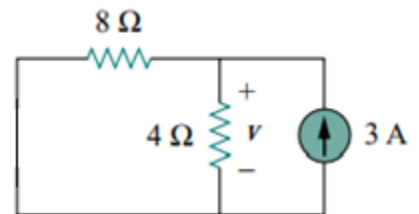


$$V = V' + V'' = 2 + 8 = 10$$

الأسئلة البعدية

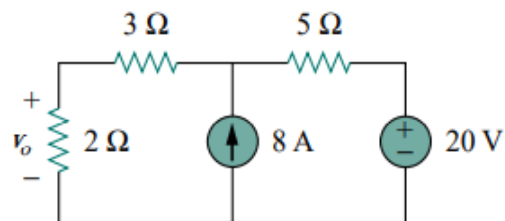- 1- Using the superposition theorem, find V_o in the circuit in Figure below (answer: $V_o=12v$)



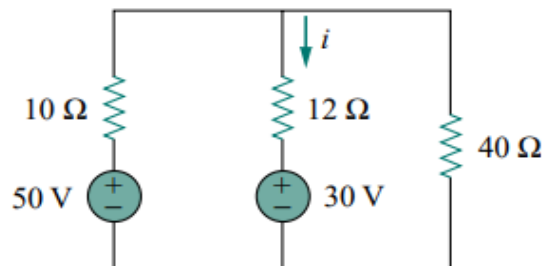- 2- determine the value i in the circuit in Figure below by Using the superposition theorem. (answer: $i=0.5A$)



رقم المحاضرة: الحادي عشر	
Thevenin's theorem	عنوان المحاضرة:
سماء خالد غانم	اسم المدرس:
المرحلة أولى\الفصل الدراسي الأول\ قسم التقنيات الإلكترونية\المعهد التقني الموصل	الفئة المستهدفة :
ان يفهم الطالب كيفية تحليل وتطبيق نظرية ثفنن في الدائرة الكهربائية	الهدف العام من المحاضرة :
1-ان يكون الطالب قادرا على تطبيق وتحليل الدائرة باستخدام نظرية ثفنن 2-ان يكون الطالب قادرا على ايجاد التيار والفولتية من خلال إيجاد الدائرة المكافئة (فولتية ثفنن و مقاومة ثفنن و المقاومة الحمل) لكل مقاومة في الدائرة باستخدام نظرية ثفنن	الأهداف السلوكية او مخرجات التعلم:
1. القاء المحاضرة 2. التعليم المدمج 3. المناقشة 4. التقارير	استر6- اتيجيات التيسير المستخدمة
7- سيتمكن الطالب من تحليل الدائرة الكهربائية التي يصعب حلها باستخدام قانون اوم 8- سيكون الطالب قادرا على تطبيق وحل الدائرة الكهربائية باستخدام نظرية ثفنن و إيجاد تيار الحمل في الدائرة الدائرة الكهربائية.	المهارات المكتسبة
امتحانات يومية-امتحانات شهرية	طرق القياس المعتمدة

الاسئلة القبليه

- Define the equivalent circuit ,Load resistance

المحتوى العلمي

- Thevenin's theorem
- Examples

محتويات المحاضرة

Thevenin's theorem


Thevenin's theorem is a way to reduce a network to equivalent circuit composed of a single voltage source, series resistance and load.

Thevenin's theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source V_{Th} in series with a resistor R_{Th} , where V_{Th} is the open-circuit voltage at the terminals and R_{Th} is the input or equivalent resistance at the terminals when the independent sources are turned off.


Steps to follow for Thevenin's theorem

- 1) Find the Thevenin source by remove the load resistance from the original circuit and calculating voltage across the open connection points where the load resistor used to be.
- 2) Find the Thevenin resistance by removing all power sources in original circuit (the voltage source is short circuit and the current source open circuit) and calculating total resistance between the open connection.
- 3) Draw the Thevenin equivalent circuit composed of a single voltage source, series resistance and load as shown in figure below.
- 4) Analyze voltage and current for the load resistor following rules for series connection such as current of load resistance I_L .

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

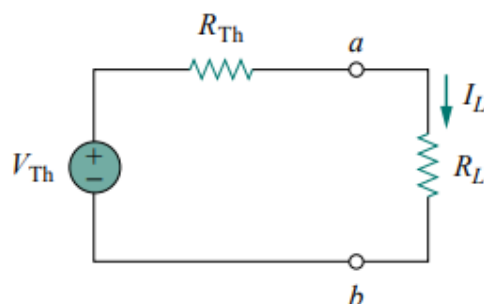

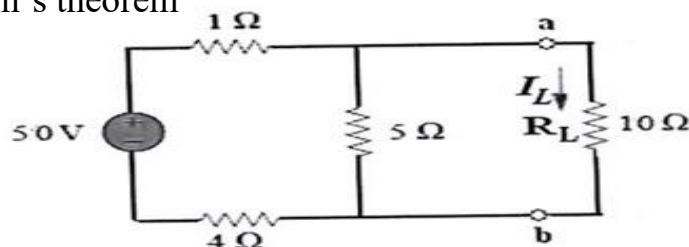
Example : Find the load current of resistance in the circuit figure below by using Thevenin's theorem



Solution:



V_{Th}

$$I = \frac{50}{1+5+4} = 5A$$

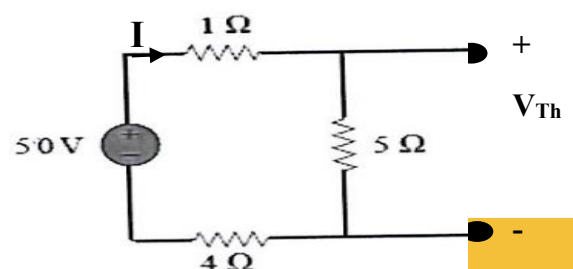

$$V_{Th} = V_{5\Omega} = 5 * 5 = 25 \text{ v}$$


$$R_{Th} = 2.5\Omega$$

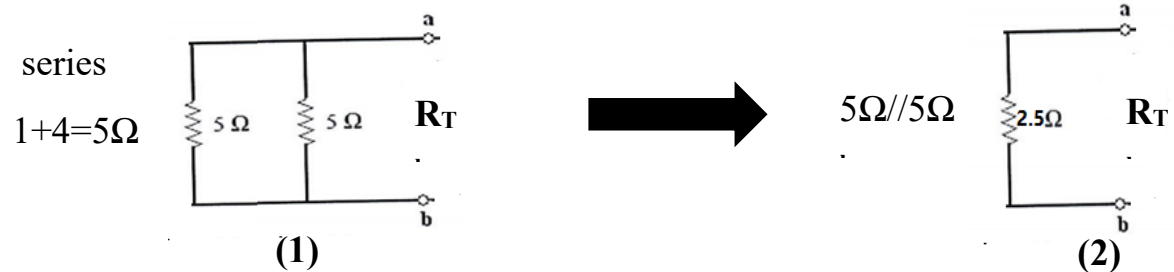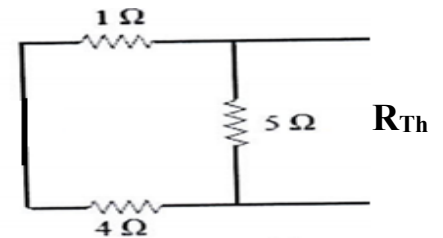


$$R_{Th} = 2.5\Omega$$

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$


$$I_L = \frac{25}{2.5 + 10} = 2A$$

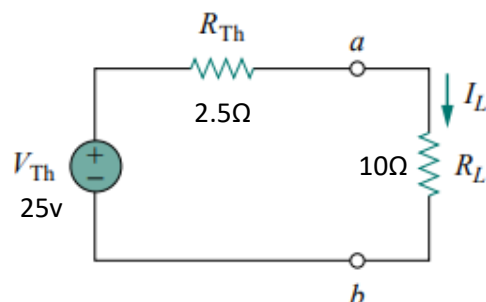

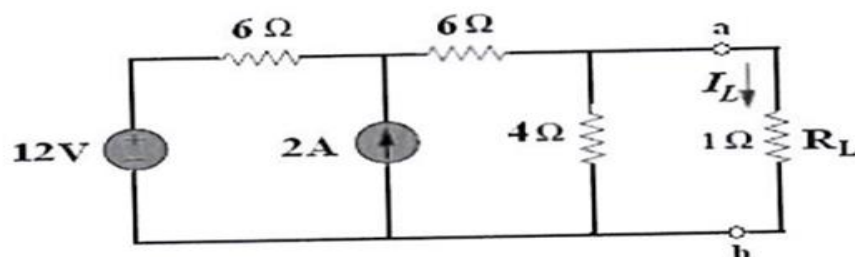Example: Find the load current of resistance in the circuit figure below by using Thevenin's theorem.



Solution:

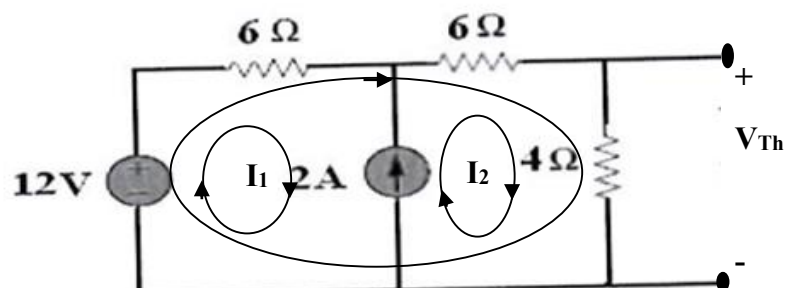

Using Mesh Method

$$I_2 - I_1 = 2$$

$$I_2 = 2 + I_1 \dots (1)$$

super loop

$$-12 + 6I_1 + 6I_2 + 4I_2 = 0$$

$$-12 + 6I_1 + 10I_2 = 0 \dots (2)$$

$$-12 + 6I_1 + 10(2 + I_1) = 0$$

$$-12 + 6I_1 + 20 + 10I_1 = 0$$

$$16 I_1 = -8$$


$$I_1 = \frac{-8}{16} = -0.5A$$

$$I_2 = 2 + I_1$$

$$I_2 = 2 + (-0.5) = 1.5$$



$$V_{Th} = V_{4\Omega} = (4 \times 1.5) = 6V$$

R_{Th}

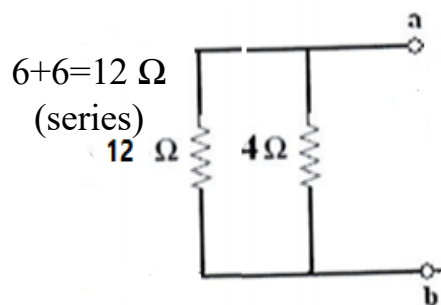


(1)

$$R_{Th} = 3\Omega$$

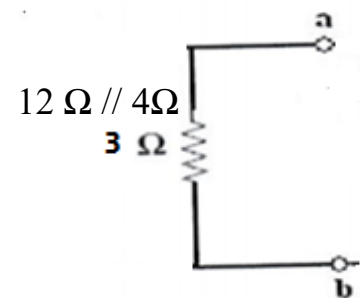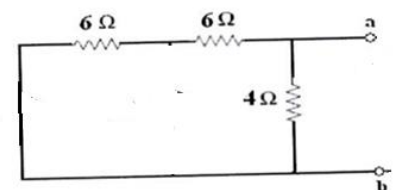

(2)

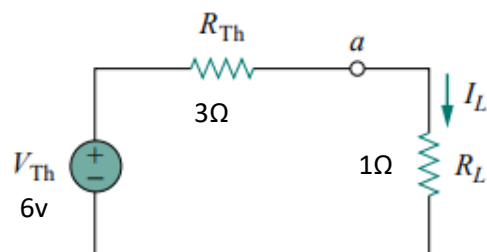

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

$$I_L = \frac{6}{3 + 1} = 1.5A$$

Example: Find the load current of resistance in the circuit figure below by using Thevenin's theorem

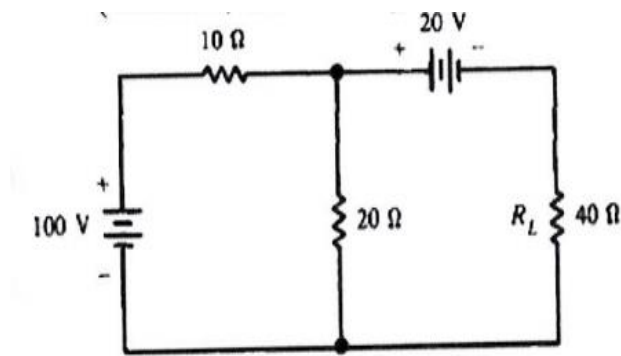


figure (6.8)

Solution

$$I = \frac{100}{10+20} = 3.33A$$

KVL:

$$-20I + 20 + V_{Th} = 0$$



$$-20 * 3.33 + 20 + V_{Th} = 0$$

$$-66.6 + 20 + V_{Th} = 0$$

$$V_{Th} = 46.6V$$


$$R_{Th} = 10\Omega // 20\Omega$$
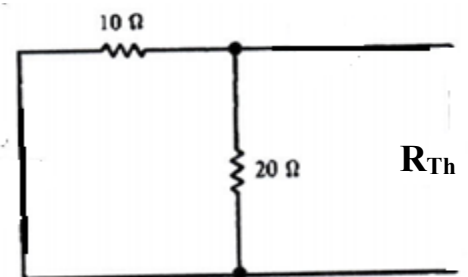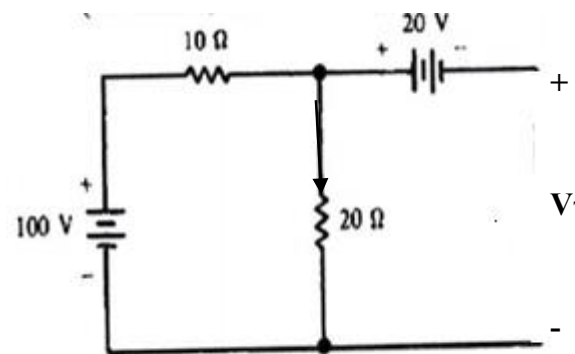
$$R_{Th} = \frac{10*20}{10+20} = 6.667\Omega$$




$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

$$I_L = \frac{46.6}{6.67 + 40} = 1A$$

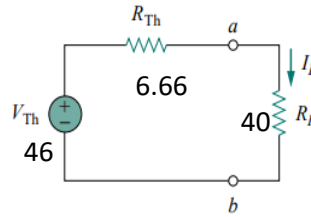


الاسئلة البعيدة

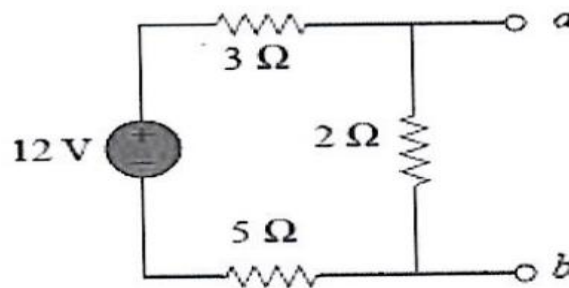- 1- Find the Thevenin equivalent of the circuit figure below. (answer: $V_{Th}=2.4v$, $R_{Th}=1.6\Omega$)



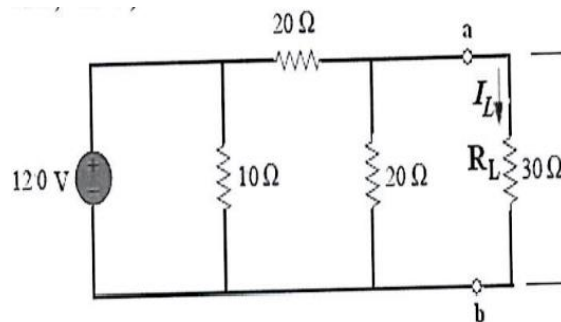- 2- Find the load current of resistance in the circuit figure below by using Thevenin's theorem. (answer: $V_{Th}=60v$, $R_{Th}=10\Omega$, $I_L = 1.5A$)



رقم المحاضرة: الثانية عشر	عنوان المحاضرة:
Norton's theorem	اسم المدرس:
سماء خالد غانم	المرحلة الأولى \ الفصل الدراسي الأول \ قسم التقنيات الإلكترونية \ المعهد التقني الموصل
ان يفهم الطالب كيفية تحليل وتطبيق نظرية نورتن في الدائرة الكهربائية	الهدف العام من المحاضرة :
1- ان يكون الطالب قادرا على تطبيق وتحليل الدائرة باستخدام نظرية نورتن 2- ان يكون الطالب قادرا على ايجاد الدائرة المكافئة (تيار نورتن ومقاومة نورتن ومقاومة الحمل) باستخدام نظرية نورتن	الأهداف السلوكية او مخرجات التعلم:
1.لقاء المحاضرة 2.التعليم المدمج 3.المناقشة 4.التقارير	استراتيجيات التيسير المستخدمة

المهارات المكتسبة	9- سيتمكن الطالب من تحليل الدائرة الكهربائية التي يصعب حلها باستخدام قانون اوم 10- سيكون الطالب قادرا على تطبيق وحل الدائرة الكهربائية نظرية نورتن و إيجاد تيار مقاومة الحمل في الدائرة الكهربائية .
طرق القياس المعتمدة	امتحانات يومية-امتحانات شهرية

الاسئلة القبليه

- Define the equivalent circuit ,Load resistance

المحتوى العلمي

- Norton's Theorem
- Examples

محتويات المحاضرة

Norton's Theorem


Norton's theorem is a way to reduce a network to equivalent circuit composed of a single current source, parallel resistance and load.

Norton's theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a current source I_N in parallel with a resistor R_N , where I_N is the short-circuit current through the terminals and R_N is the input or equivalent resistance at the terminals when the independent sources are turned off.


Steps to follow for Norton's theorem

- 1) Find the Thevenin source by remove the load resistance from the original circuit and calculating voltage across the open connection points where the load resistor used to be.
- 2) Find the Norton resistance by removing all power sources in original circuit (the voltage source is short circuit and the current source open circuit) and calculating total resistance between the open connection.
- 3) Draw the Norton equivalent circuit composed of a single current source, parallel resistance and load as shown in figure below.
- 4) Analyze voltage and current for the load resistor following rules for parallel connection such as current of load resistance I_L .

$$I_L = \frac{I_N}{R_N + R_L} * R_N$$

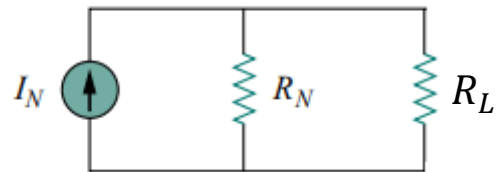


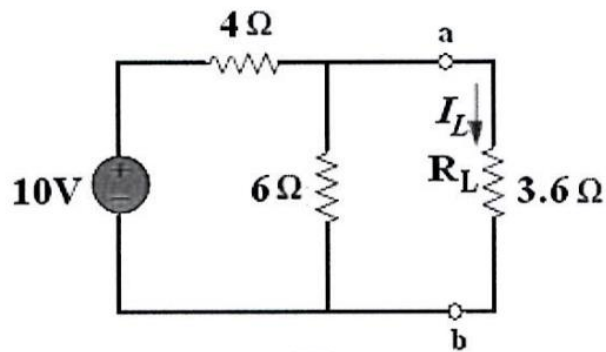Example : Find the load current of resistance in the circuit figure below by using Norton's theorem.




Solution:

$$I_N = \frac{10}{4} = 2.5\text{A}$$

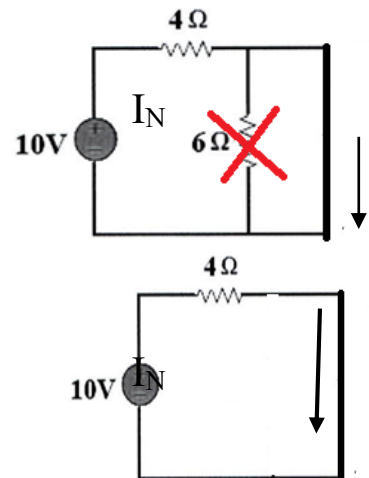

Find R_N
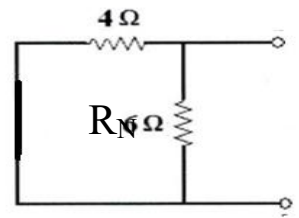
$$4\Omega // 6\Omega = \frac{4*6}{4+6} = 2.4\Omega$$




Norton Equivalent


$$I_L = \frac{I_N}{R_N + R_L} * R_N$$

$$I_L = \frac{2.5}{2.4 + 3.6} * 2.4$$

$$I_L = 1A$$

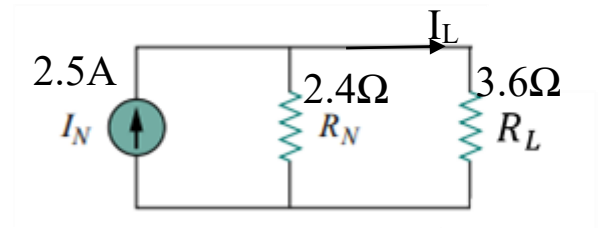

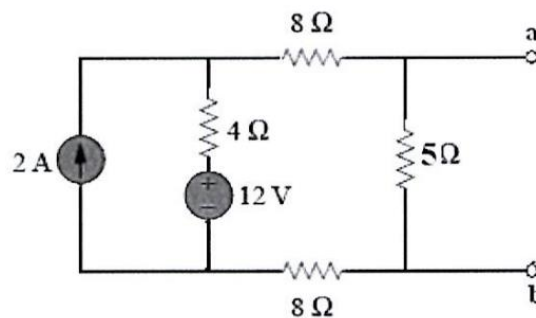Example: In the circuit figure below Find Norton equivalent circuit.



Solution:

$$I_1 = 2A$$

$$-12 + 4(I_2 - I_1) + 8I_2 + 8I_2 = 0 \quad (\text{loop 2})$$



$$-12 + 4I_2 - 4I_1 + 16I_2 = 0$$

$$-12 - (4 * 2) + 20I_2 = 0$$

$$-20 + 20I_2 = 0$$

$$I_2 = 1A$$


$$I_2 = I_N = 1A$$

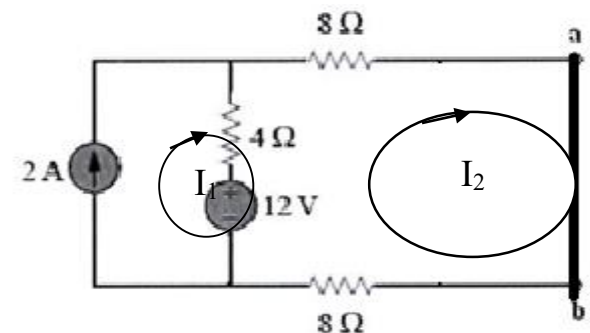
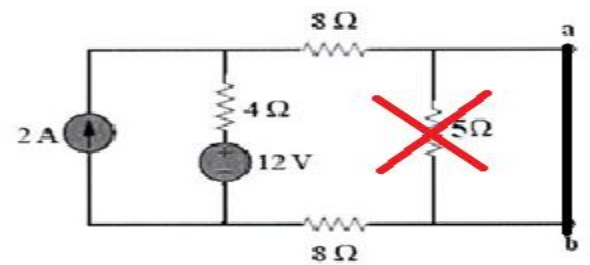


$$R_N$$

$$4 + 8 + 8 = 20\Omega$$


$$20\Omega // 5\Omega = 4\Omega$$

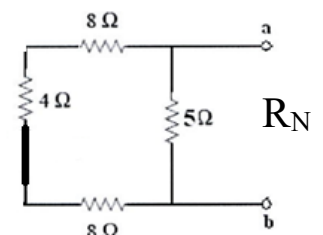

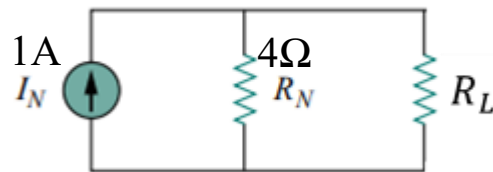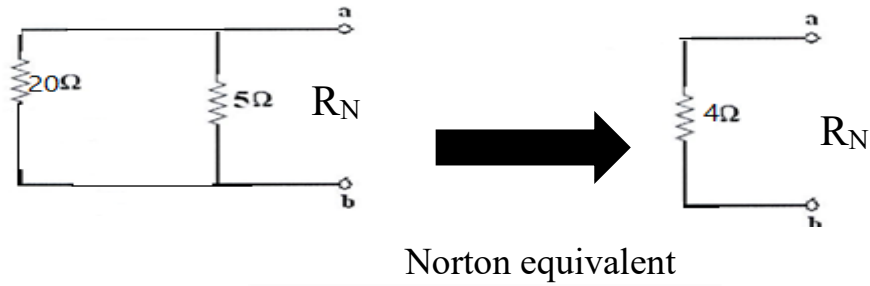

الأسئلة البعدية

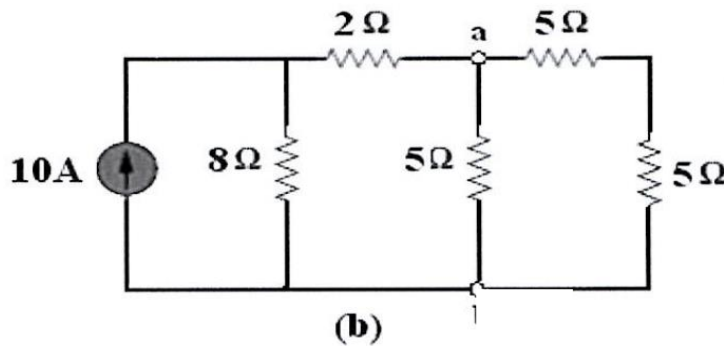Find the current of load resistance in the circuit figure below using Norton's theorem. (answer: $I_N=8A$ $R_N=5\Omega$, $I_L=4A$)




رقم المحاضرة: الثالثة عشر	Source transformations
عنوان المحاضرة:	سماء خالد غانم
اسم المدرس:	المرحلة أولى\الفصل الدراسي الأول\ قسم التقنيات الإلكترونية\المعهد التقني الموصل
الفئة المستهدفة :	ان يفهم الطالب كيفية تحويل المصادر لحل الدائرة الكهربائية
الهدف العام من المحاضرة :	1-ان يكون الطالب قادرا على تطبيق وتحليل الدائرة باستخدام تحويل المصادر 2-ان يكون الطالب قادرا على ايجاد الفولتية او التيار للمقاومة المطلوبة في الدائرة الكهربائية باستخدام تحويل المصادر
الأهداف السلوكية او مخرجات التعلم:	1.لقاء المحاضرة 2.التعليم المدمج 3.المناقشة 4.التقارير
استراتيجيات التيسير المستخدمة	11- سيتمكن الطالب من تحليل الدائرة الكهربائية التي يصعب حلها باستخدام قانون اوم
المهارات المكتسبة	

12- سيكون الطالب قادرا على تطبيق وحل الدائرة الكهربائية باستخدام تحويل المصادر .	
امتحانات يومية-امتحانات شهرية	طرق القياس المعتمدة

الاسئلة القليلة

use the superposition theorem to find i

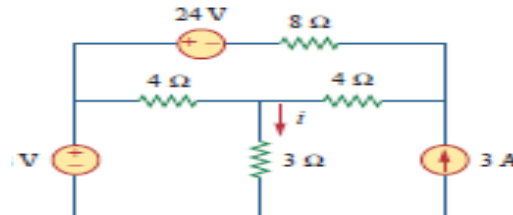


المحتوى العلمي

- Source transformation
- Example

محتويات المحاضرة

Source Transformation:

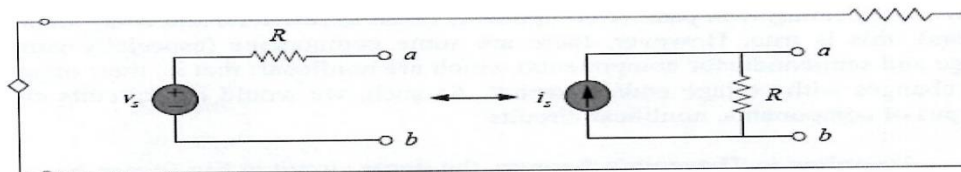
We have noticed that series-parallel combination and wye-delta transformation help simplify circuits. Sources transformation is another tool for simplifying circuits. Basic to these tools is the concept of equivalence.



A source transformation is the process of replacing a voltage source v_s in series with a resistor R by a current source i_s in parallel with a resistor R , or vice versa.

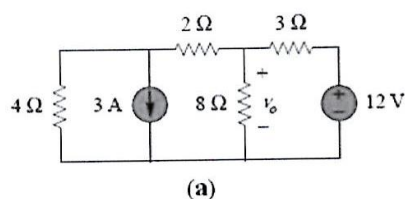
Example

Use source transformation to find V_o to circuit in Fig. (a). (Ans. 3.2 V).



الأسئلة البعدي

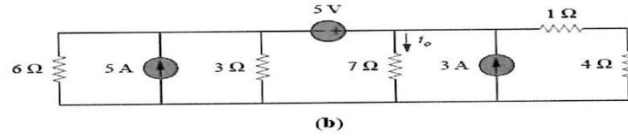
Find I_o in the circuit of Fig. (b) using source transformation. (Ans. $1/8 \text{ A}$)



رقم المحاضرة: الرابعة عشر	عنوان المحاضرة:
اسم المدرس:	سماء خالد غانم
الفئة المستهدفة:	المرحلة الأولى \ الفصل الدراسي الأول \ قسم التقنيات الإلكترونية \ المعهد التقني الموصل
الهدف العام من المحاضرة:	ان يفهم الطالب كيفية إيجاد اعظم قدرة في مقاومة الحمل في الدائرة الكهربائية
الأهداف السلوكية او مخرجات التعلم:	ان يكون الطالب قادرا على تطبيق وتحليل الدائرة باستخدام نظرية ثفنن وإيجاد اعظم نقل قدرة في مقاومة الحمل في الدائرة الكهربائية
استراتيجيات التيسير المستخدمة	1.لقاء المحاضرة 2.التعليم المدمج 3.المناقشة 4.التقارير
المهارات المكتسبة	سيكون الطالب قادرا على تطبيق و حل الدائرة الكهربائية وإيجاد اعظم نقل قدرة.
طرق القياس المعتمدة	امتحانات يومية – امتحانات شهرية

الاسئلة القبليّة

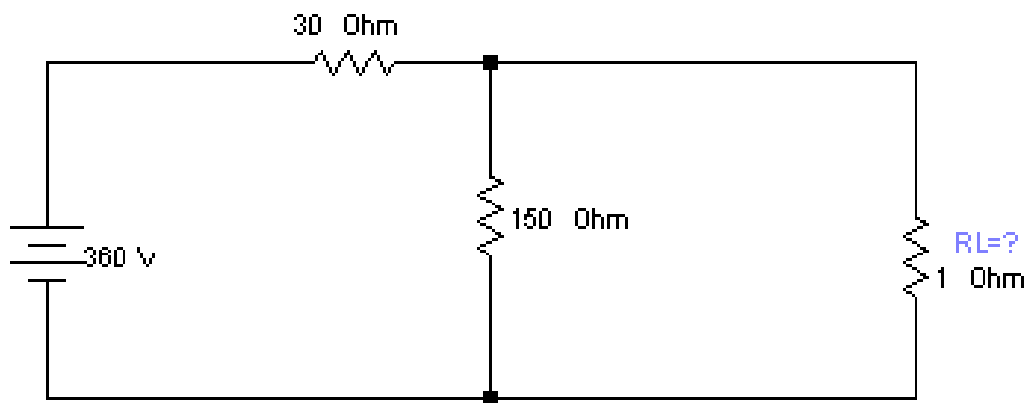Find the current in the load resistance using Thevenin's theorem



المحتوى العلمي

- Maximum power transfer theorem
- Example

7 Maximum power transfer theorem:

In many practical situations, a circuit is designed to provide power to a load. While for electric utilities, minimizing power losses in the process of transmission and distribution is critical for efficiency and economic reasons, there are other applications in areas such as communications where it is desirable to maximize the power delivered to a load. We now address the problem of delivering the maximum power to a load when given a system with known internal losses. It should be noted that this will result in significant internal losses greater than or equal to the power delivered to the load.

The Thevenin equivalent is useful in finding the maximum power a linear circuit can deliver to a load. We assume that we can adjust the load resistance R_L .

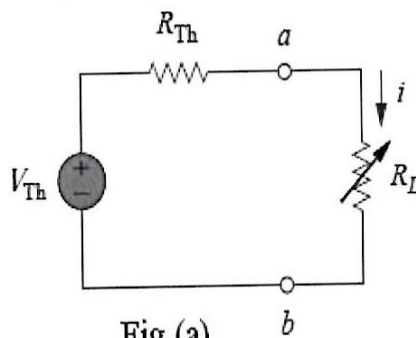


Fig. (a)


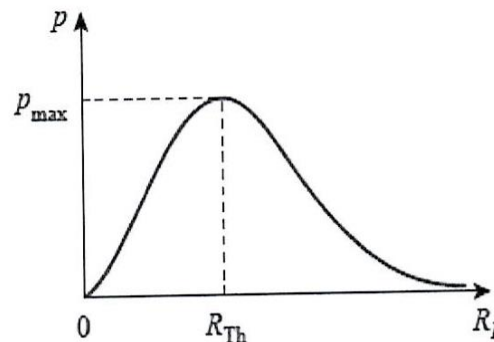


Fig. (b)

For a given circuit Fig. (a), V_{Th} and R_{Th} are fixed. By varying the load resistance R_L , the power delivered to the load varies as sketched in Fig. b. We notice from Fig. b that the power is small for small or large values of R_L but maximum for some value of R_L between 0 and ∞ . We now want to show that this maximum power occurs when R_L is equal to R_{Th} . This is known as the *maximum power theorem*.

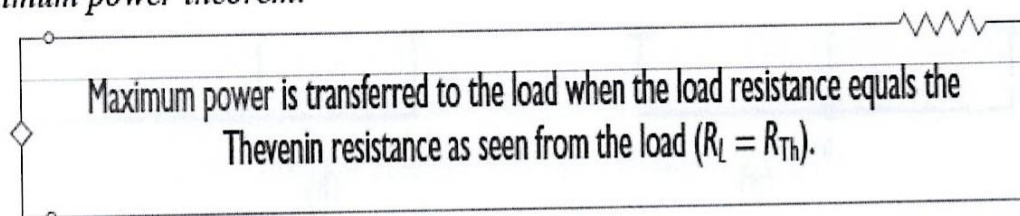

Taking our Thevenin equivalent example circuit, the Maximum Power Transfer Theorem tells us that the load resistance resulting in greatest power dissipation is equal in value to the Thevenin resistance (in this case, 0.8Ω) Fig. 35:

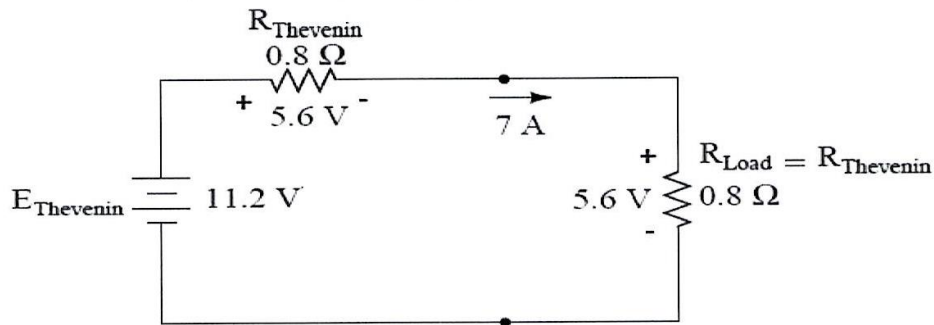


Fig. 35


With this value of load resistance, the dissipated power will be 39.2 watts:

REVIEW:

The Maximum Power Transfer Theorem states that the maximum amount of power will be dissipated by a load resistance if it is equal to the Thevenin or Norton resistance of the network supplying power.

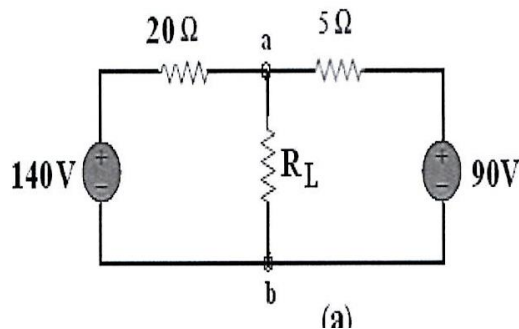
Example

Find the value of load resistance R_L that will provide the maximum power delivered to the load Fig. (a). Also calculate maximum power P_L . (Ans. 4Ω , 625W)



(a)

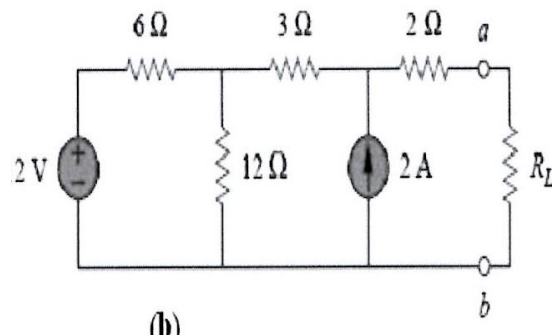Find the value of R_L for maximum power transfer in the circuit of Fig. (b). Find the maximum power. (Ans. 9Ω , 13.44W)



(b)

المصادر الأساسية:

- 1- Charles K. Alexander, Mathew N. O. Sadiku "Fundamental of electric circuit", 3rd.
- 2- Road M. Rasheed, "Lectures electric circuit", Part1.